

# ***Basics in Verilog Design***

- |  |  |
|--|--|
| 1.Logic Gates using Gate Level model       | 26.Binary-Seven Segment Display Converter        |
| 2.Logic Gates using Data model             | 27.Carry Look Ahead Adder                        |
| 3.Half Adder                               | 28.BCD Adder                                     |
| 4.Full Adder                               | 29.BCD-Excess_3 Converter                        |
| 5.Full Adder using Half adders             | 30.Carry Save Adder                              |
| 6.Half Subtractor                          | 31.Squares of 3bit numbers                       |
| 7.Full Subtractor                          | 32.Tristate Buffer                               |
| 8.Full Subtractor using Half Subtractors   | 33.RS Latch using NOR gates                      |
| 9.Ripple Carry Adder(4-bit)                | 34.RS Latch using NAND gates                     |
| 10.Multiplexer(2*1)                        | 35.SR Flipflop                                   |
| 11.Multiplexer(8*1)                        | 36.JK Flipflop                                   |
| 12.Multiplexer(8*1) using Multiplexer(2*1) | 37.D Flipflop                                    |
| 13.DeMultiplexer(1*8)                      | 38.T Flipflop                                    |
| 14.Encoder(8*3)                            | 39.D Latch                                       |
| 15.Priority Encoder                        | 40.Asynchronous counter using T Flipflops        |
| 16. 4-bit Comparator                       | 41.Synchronous Up and Down Counter               |
| 17.Decimal-BCD Encoder                     | 42.Johnson Counter                               |
| 18.Octal-Binary Encoder                    | 43.Ring Counter                                  |
| 19.Hexadecimal-Binary Encoder              | 44.Serial In Serial Out Shift Register(SISO)     |
| 20.Binary-Gray Converter                   | 45.Serial In Parallel Out Shift Register(SIPO)   |
| 21.Gray-Binary Converter                   | 46.Parallel In Serial Out Shift Register(PISO)   |
| 22.Even Parity Generator                   | 47.Parallel In Parallel Out Shift Register(PIPO) |
| 23.Odd Parity Generator                    | 48.Master-Slave D Flipflop                       |
| 24.Even Parity Checker                     | 49.Sequence Detector using Mealy FSM             |
| 25.Odd Parity Checker                      | 50.Sequence Detector using Moore FSM             |


# **1.Logic Gates using Gate Level model**

## **Verilog Code:**

```
module gate_logic(a,b,and_out,or_out,nand_out,nor_out,notb_out,xor_out,xnor_out);
input a,b;
output and_out,or_out,nand_out,nor_out,notb_out,xor_out,xnor_out;
and a1 (and_out,a,b);
or o1(or_out,a,b);
nand n1(nand_out,a,b);
nor n2(nor_out,a,b);
not n3(notb_out,b);
xor x1(xor_out,a,b);
xnor x2 (xnor_out,a,b);
endmodule
```
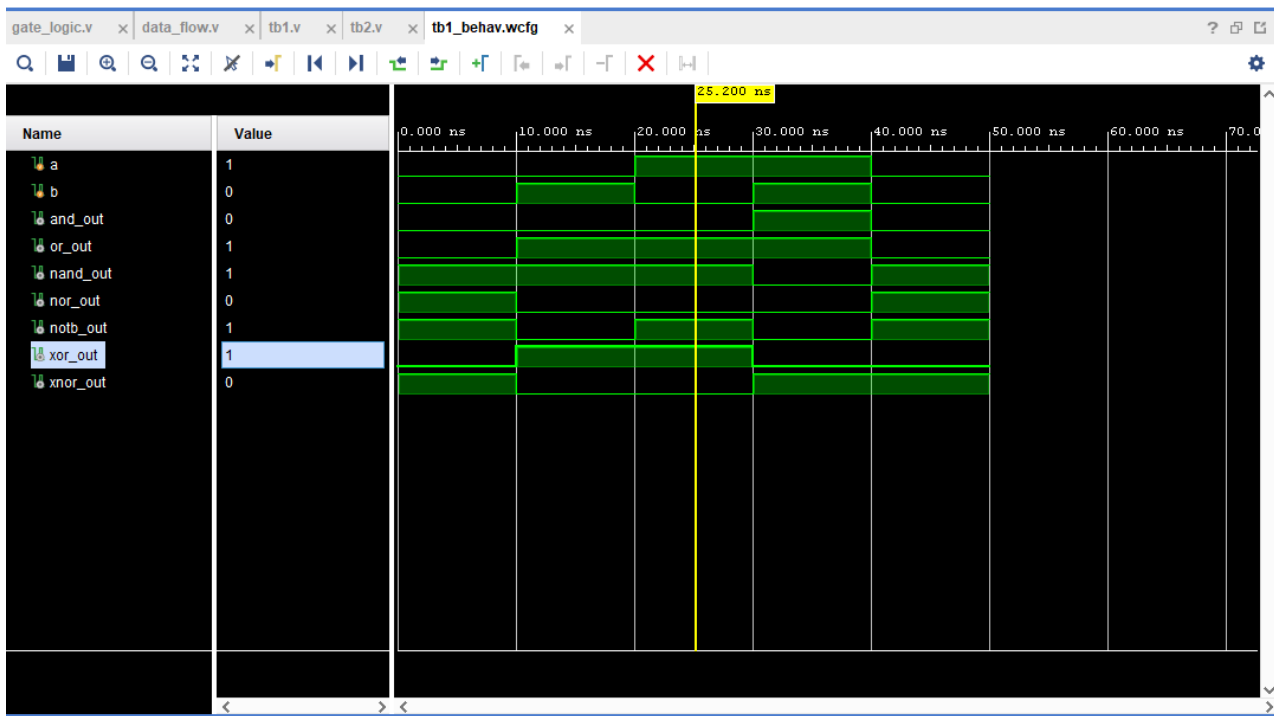
## **Test Bench:**

```
module tb1( );
reg a,b;
wire and_out,or_out,nand_out,nor_out,notb_out,xor_out,xnor_out;
gate_logic uut(
    .a(a),
    .b(b),
    .and_out(and_out),
    .or_out(or_out),
    .notb_out(notb_out),
    .nand_out(nand_out),
    .nor_out(nor_out),
    .xor_out(xor_out),
    .xnor_out(xnor_out)
);
initial
begin
    a=0; b=0; #10
    a=0; b=1; #10
    a=1; b=0; #10
    a=1; b=1; #10
    a=0; b=0; #10
    $finish;
end
endmodule
```



## 2.Logic Gates using Data model

### Verilog Code:

```
module data_flow(a,b,and_out,or_out,nand_out,nor_out,notb_out,xor_out,xnor_out);
input a,b;
output and_out,or_out,nand_out,nor_out,notb_out,xor_out,xnor_out;
assign and_out=a&b;
assign or_out=a|b;
assign nand_out=~(a&b);
assign nor_out=~(a|b);
assign notb_out=~b;
assign xor_out=a^b;
assign xnor_out=~(a^b);
endmodule
```

### Test Bench:

```
module tb2( );
reg a,b;
wire and_out,or_out,nand_out,nor_out,notb_out,xor_out,xnor_out;

data_flow uut(
    .a(a),
    .b(b),
    .and_out(and_out),
    .or_out(or_out),
    .notb_out(notb_out),
    .nand_out(nand_out),
    .nor_out(nor_out),
```

```


.xor_out(xor_out),
.xnor_out(xnor_out)
);

```

```

initial
begin
    a=0; b=0; #10
    a=0; b=1; #10
    a=1; b=0; #10
    a=1; b=1; #10
    a=0; b=0; #10
    $finish;
end
endmodule

```

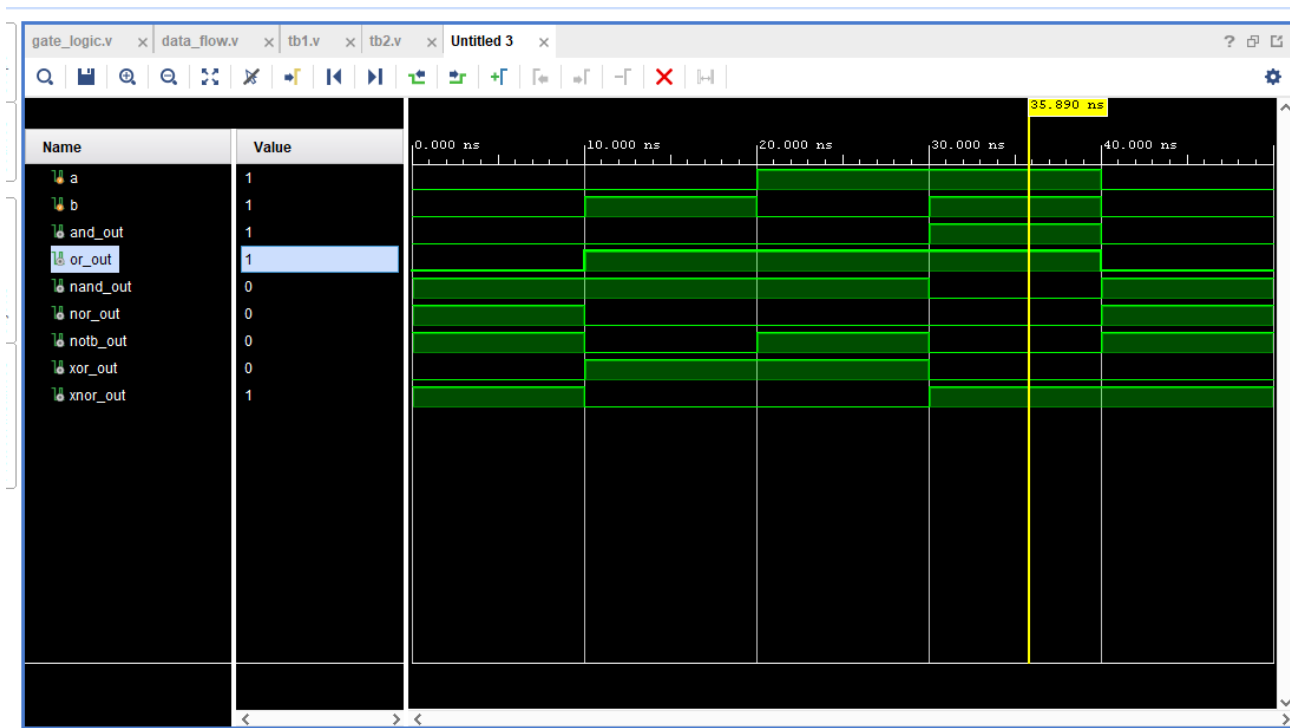

### 3.Half Adder

#### Verilog Code:


```

module half_adder(input a,b ,
output sum, carry );
    assign sum=a^b;
    assign carry= a&b;
endmodule

```
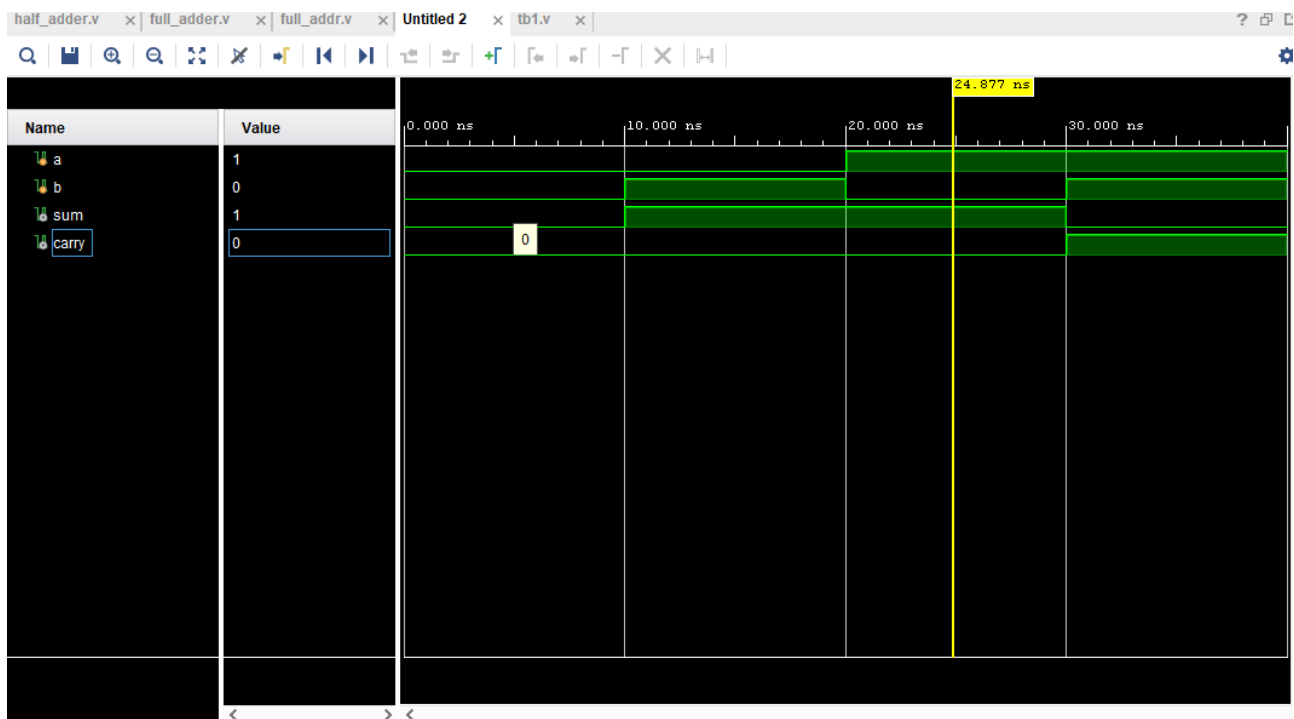
### Test Bench:

```
module tb1();
reg a,b; wire sum,carry;
half_adder uut(a,b,sum,carry);
initial
begin
a=0;b=0; #10
a=0;b=1; #10
a=1;b=0; #10
a=1;b=1;#10
$finish;
end
endmodule
```




## 4.Full Adder

### Verilog Code:

```
module full_adder(input a,b,c,output sum, carry);
assign sum= a^b^c;
assign w1=a&b;
assign w2=b&c;
assign w3=a&c;
assign carry=w1|w2|w3;
endmodule
```
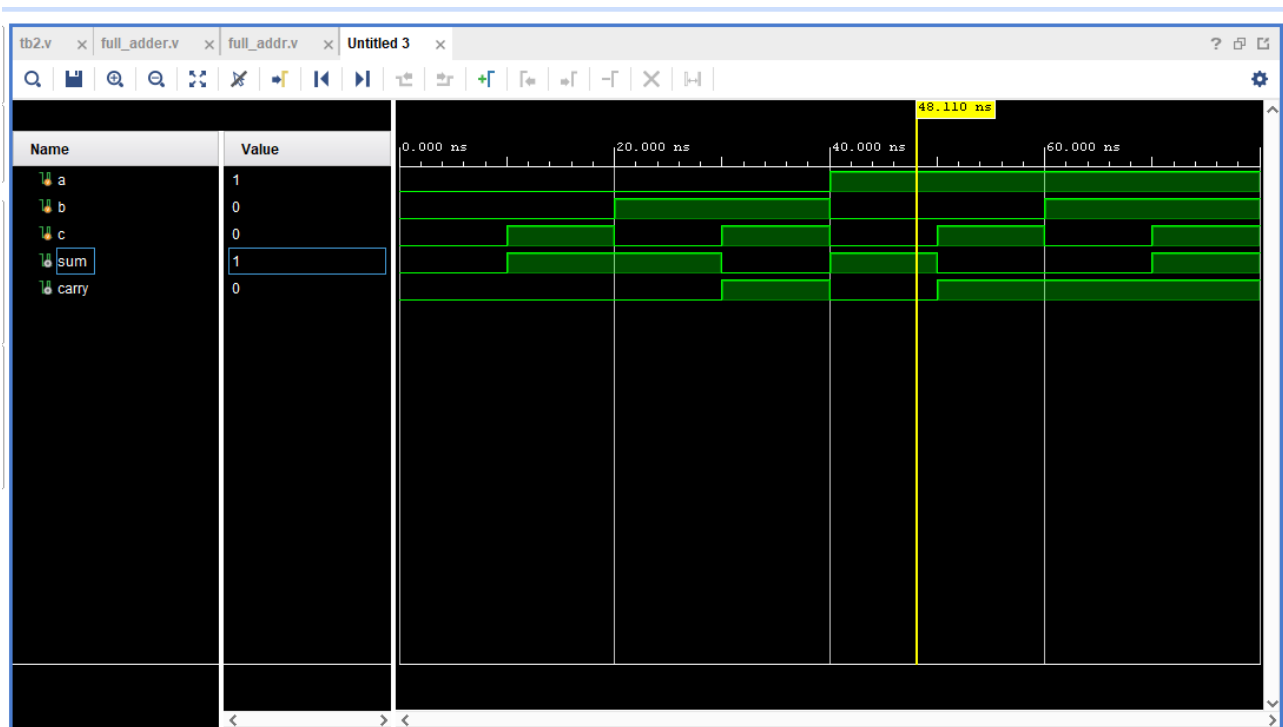
### TestBench:

```
module tb2();
reg a,b,c; wire sum,carry;
full_adder uut(a,b,c ,sum,carry);
initial
begin
a=0;b=0;c=0; #10
a=0;b=0;c=1; #10
a=0;b=1;c=0; #10
a=0;b=1;c=1; #10
a=1;b=0;c=0; #10
a=1;b=0;c=1; #10
a=1;b=1;c=0; #10
a=1;b=1;c=1; #10
$finish;
end
endmodule
```



## 5.Full Adder using Half adders


### Verilog Code:

```
module full_addr(input a,b,c, output sum, carry);
half_adder h1(a,b,w1,w2);
half_adder h2(w1,c,sum,w3);
```

```
assign carry=w2|w3;
endmodule
```
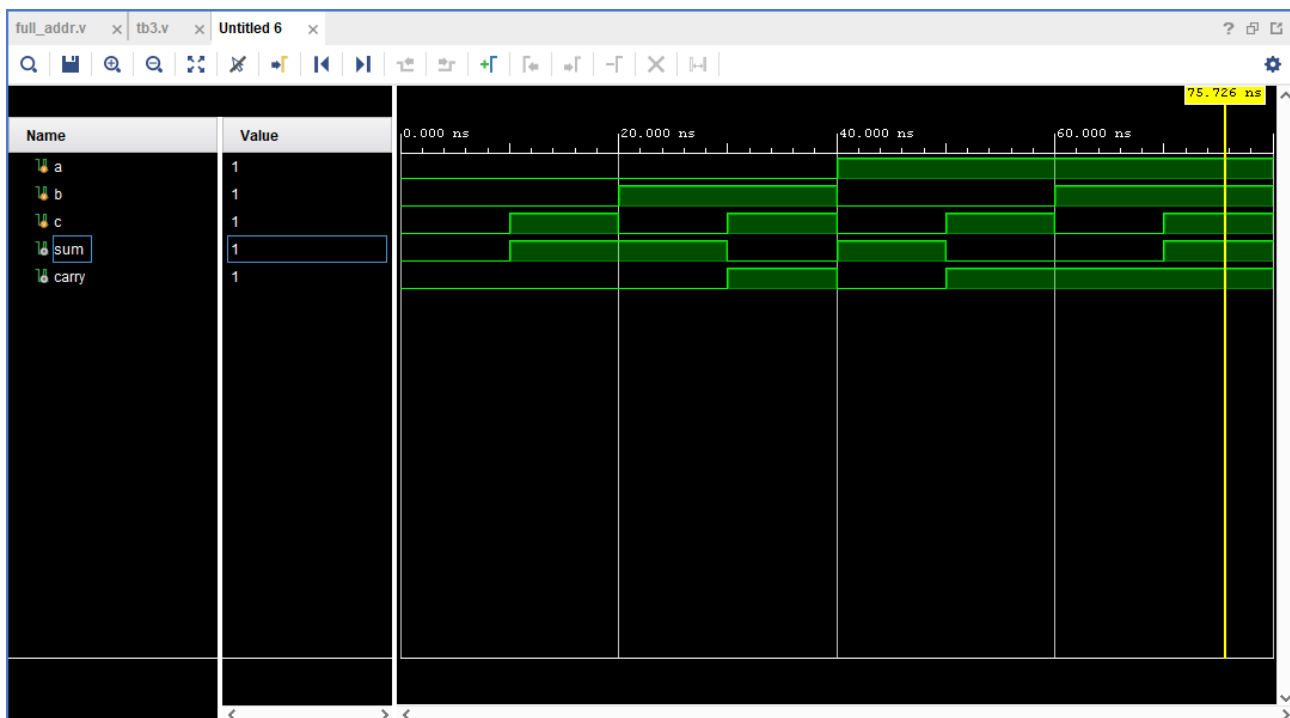
### TestBench:

```
module tb3();
reg a,b,c; wire sum,carry;
full_addr uut(a,b,c,sum,carry);
initial
begin
for ( integer count = 0; count < 8; count = count + 1)
begin
{a, b, c}= count[2:0];
#10;
end
$finish;
end
endmodule
```




## 6. Half Subtractor

### Verilog Code:

```
module half_subtractor( input a,b,output d,bo);
assign d=a^b;
assign bo=(~a)&b;
endmodule
```
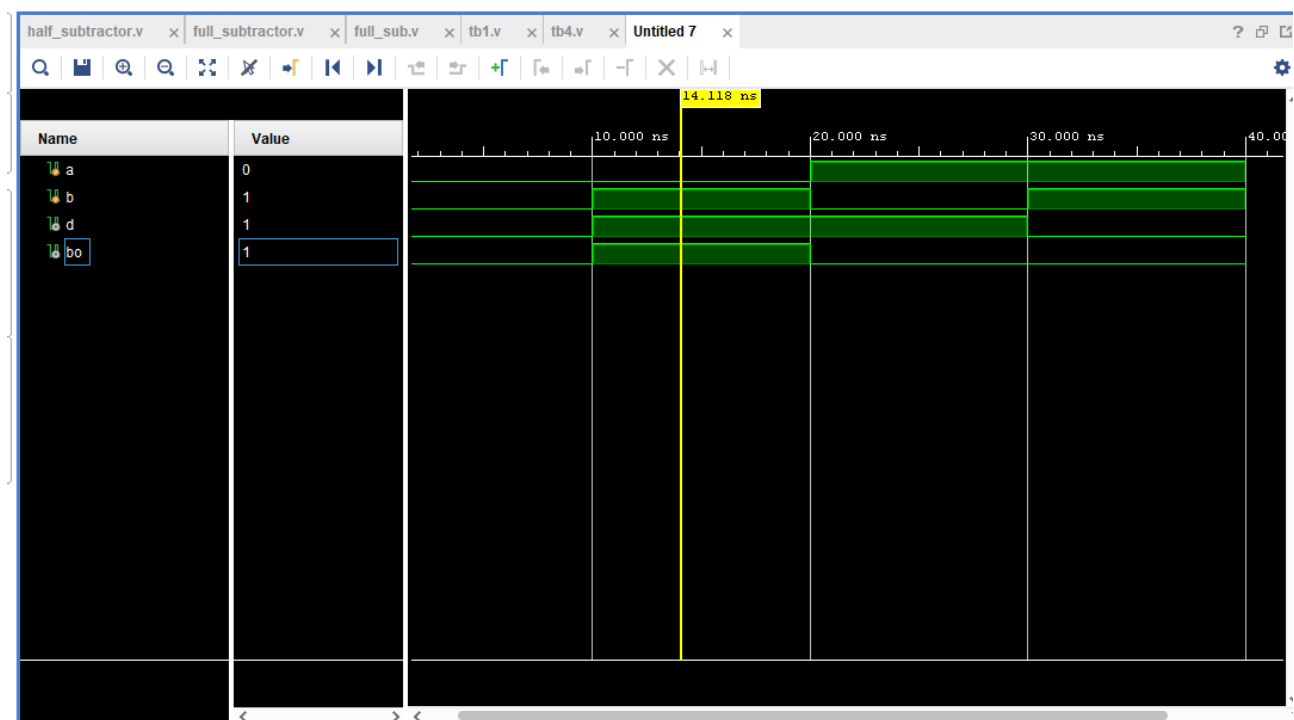
### TestBench:

```
module tb4();
reg a,b; wire d,bo;
half_subtractor uut(a,b,d,bo);
initial
begin
a=0;b=0; #10
a=0;b=1; #10
a=1;b=0; #10
a=1;b=1;#10
$finish;
end
endmodule
```



## 7.Full Subtractor

### Verilog Code:

```
module full_subtractor(input a,b,c ,output d, bo );
assign d=a^b^c;
assign w1=(~a)&b;
assign w2=(~a)&c;
assign w3=b&c;
assign bo= w1|w2|w3;
endmodule
```

### TestBench:

```
module tb5( );
reg a,b,c ; wire d, bo;
```




```

full_subtractor uut(a,b,c ,d,bo);
initial
begin
a=0;b=0;c=0; #10
a=0;b=0;c=1; #10
a=0;b=1;c=0; #10
a=0;b=1;c=1; #10
a=1;b=0;c=0; #10
a=1;b=0;c=1; #10
a=1;b=1;c=0; #10
a=1;b=1;c=1; #10
$finish;
end
endmodule

```
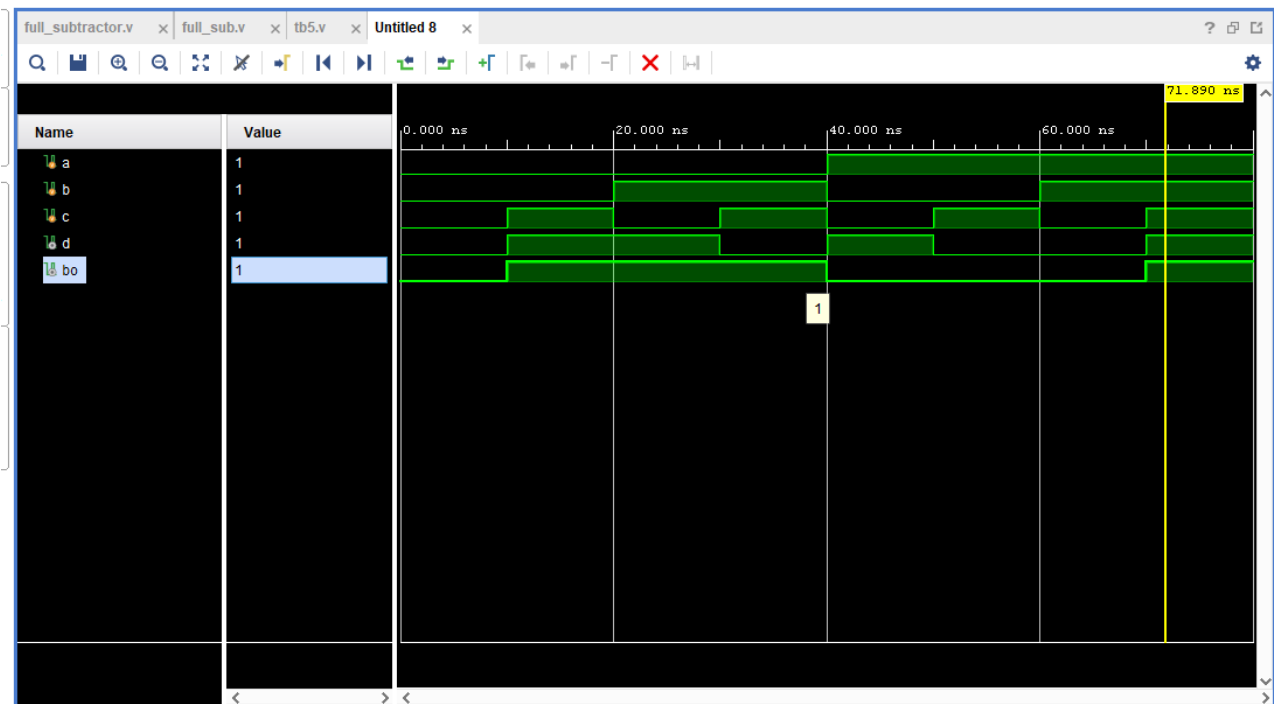
## 8.Full Subtractor using Half Subtractors



### Verilog Code:

```

module full_sub(input a,b,c,output d,bo);
half_subtractor h1(a,b,w1,w2);
half_subtractor h2(w1,c,d,w3);
assign bo= w2|w3;
endmodule

```

### TestBench:

```


module tb6( );
reg a,b,c; wire d,bo;
full_sub uut(a,b,c ,d,bo);

```

```

initial
begin
a=0;b=0;c=0; #10
a=0;b=0;c=1; #10
a=0;b=1;c=0; #10
a=0;b=1;c=1; #10
a=1;b=0;c=0; #10
a=1;b=0;c=1; #10
a=1;b=1;c=0; #10
a=1;b=1;c=1; #10
$finish;
end
endmodule

```

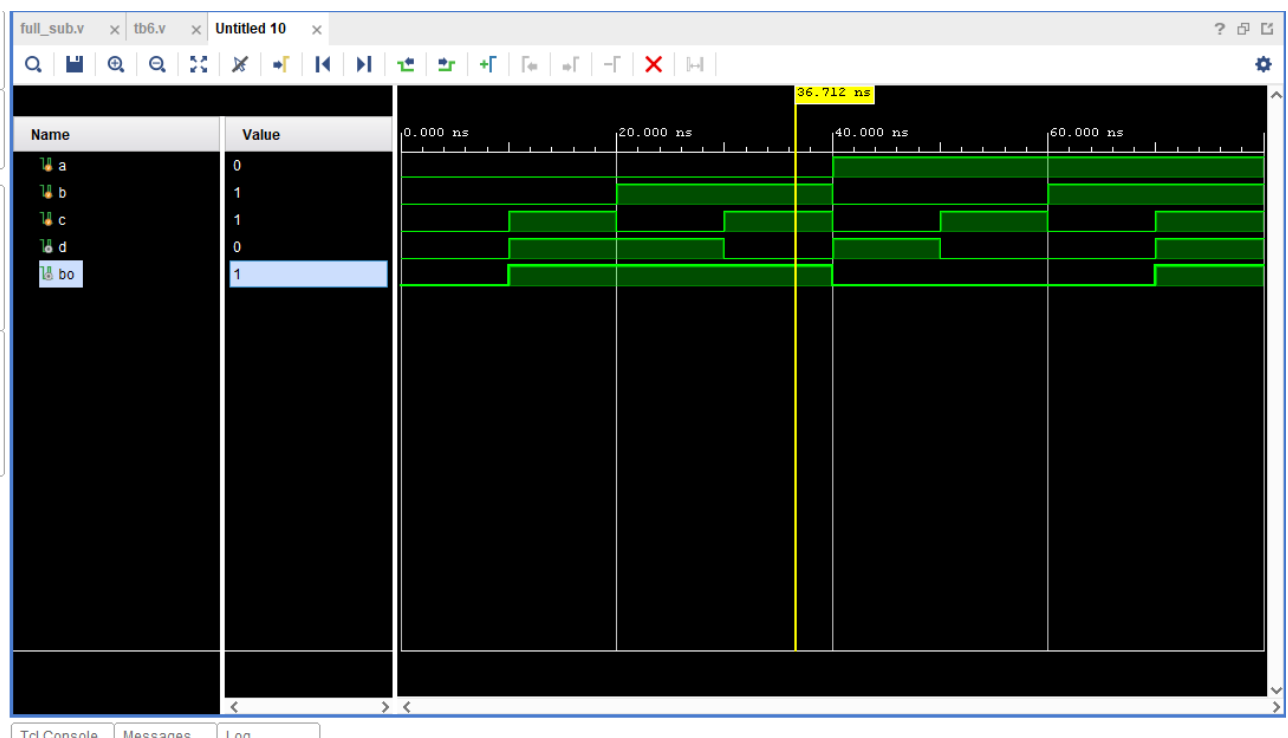

## 9.Ripple Carry Addder(4-bit)

### Verilog Code:

```


module ripple_carry_addr(a,b,cin, sum,carry );
input [3:0] a,b;
input cin;
output [3:0] sum;
output carry;
wire[2:0] c;
full_adder f1(a[0],b[0],cin,sum[0],c[0]);
full_adder f2(a[1],b[1],c[0],sum[1],c[1]);
full_adder f3(a[2],b[2],c[1],sum[2],c[2]);

```

```
full_adder f4(a[3],b[3],c[2],sum[3],carry);
endmodule
```
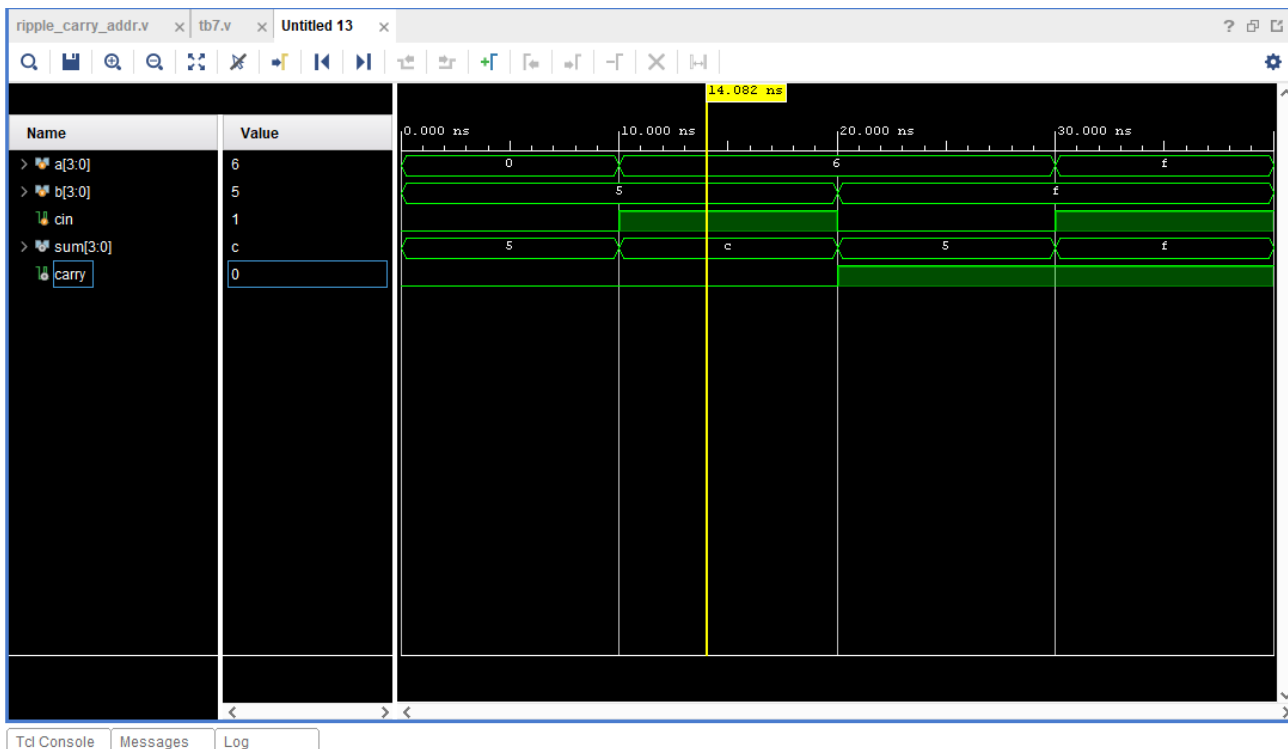
### TestBench:

```
module tb7();
reg [3:0] a,b; reg cin; wire [3:0] sum; wire carry;
ripple_carry_adder uut (a,b, cin,sum,carry);
initial begin
a=4'b0000; b=4'b0101; cin=0; #10
a=4'b0110; b=4'b0101; cin=1; #10
a=4'b0110; b=4'b1111; cin=0; #10
a=4'b1111; b=4'b1111; cin=1; #10
$finish;
end
endmodule
```



## 10. Multiplexer(2\*1)

### Verilog Code:

```
module x1_mux(a,b,s,out);
input a,b,s;
output out;
assign out=((~s)&a)|(s&b);
endmodule
```


### TestBench:

```
module tb1();
reg a,b,s; wire out;
```

```

x1_mux uut(a,b,s,out);
initial
begin
a=0;b=1; s=0; #10
a=0;b=1; s=1; #10
a=1;b=0; s=0; #10
a=1;b=0; s=1; #10
$finish;
end
endmodule

```

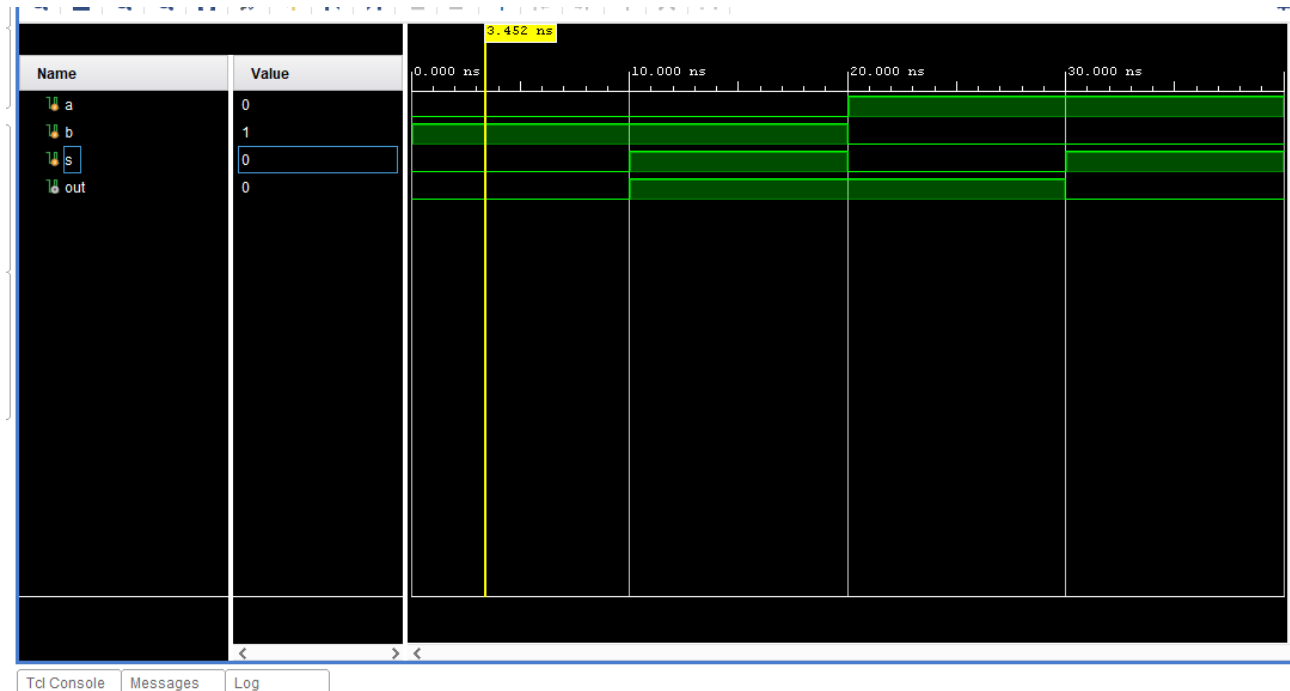

## 11. Multiplexer(8\*1)

### Verilog Code:

```


module eight_x_one_mux(in,sel,out );
input [7:0] in;
input [2:0] sel;
output reg out;
always @ (*)
begin
case(sel)
3'b000: out=in[0];
3'b001: out=in[1];
3'b010: out=in[2];
3'b011: out=in[3];
3'b100: out=in[4];
3'b101: out=in[5];
3'b110: out=in[6];

```

```
3'b111: out=in[7];
default: out=0;
endcase
end
endmodule
```
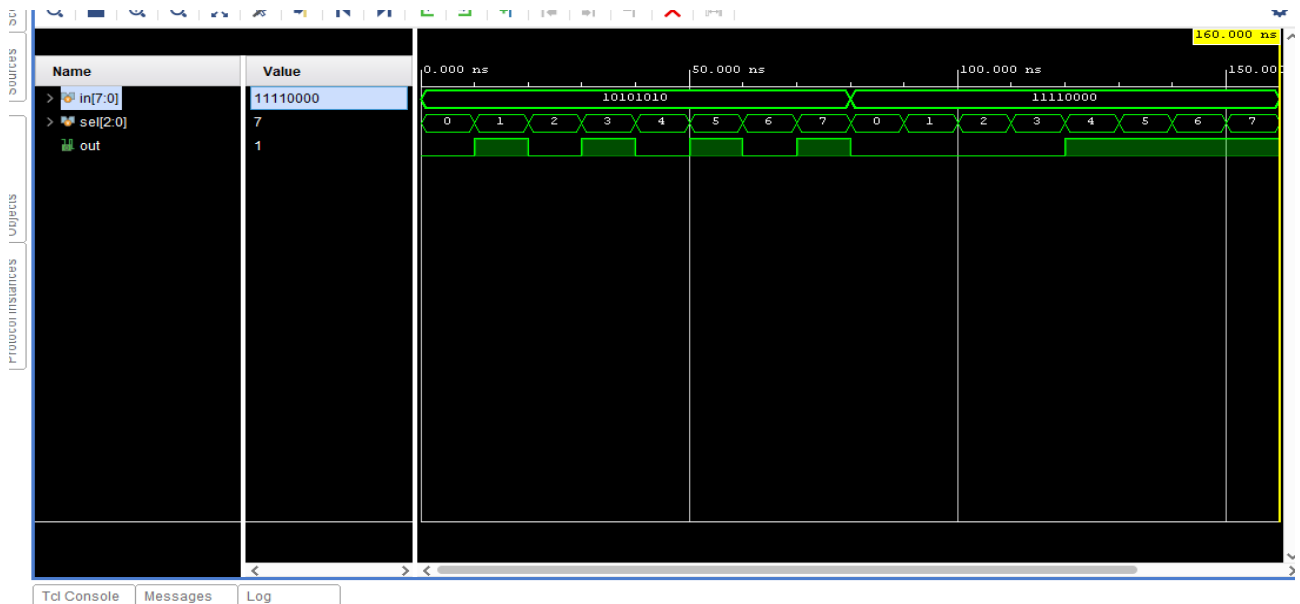
### **TestBench:**

```
module tb3(out);
reg [7:0] in;
reg [2:0] sel;
output out;
eight_x_one_mux dut (in,sel,out);
initial
begin
in=8'b10101010;
sel=3'b000; #10
sel=3'b001; #10
sel=3'b010; #10
sel=3'b011; #10
sel=3'b100; #10
sel=3'b101; #10
sel=3'b110; #10
sel=3'b111; #10
in=8'b11110000;
sel=3'b000; #10
sel=3'b001; #10
sel=3'b010; #10
sel=3'b011; #10
sel=3'b100; #10
sel=3'b101; #10
sel=3'b110; #10
sel=3'b111; #10
$finish;
end
endmodule
```



## 12. Multiplexer(8\*1) using Multiplexer(2\*1)

### Verilog Code:

```

module x8(in,sel,out);
input [7:0]in;
input [2:0] sel;
output out;
x1_mux m1(in[0],in[1],sel[0],w1);
x1_mux m2(in[2],in[3],sel[0],w2);
x1_mux m3(in[4],in[5],sel[0],w3);
x1_mux m4(in[6],in[7],sel[0],w4);
x1_mux m5(w1,w2,sel[1],w5);
x1_mux m6(w3,w4,sel[1],w6);
x1_mux m7(w5,w6,sel[2],out);
endmodule

```

### TestBench:

```

module tb2(out);
reg [7:0] in;
reg [2:0] sel;
output out;
x8 dut (in,sel,out);
initial
begin
in=8'b10101010;
sel=3'b000; #10
sel=3'b001; #10
sel=3'b010; #10
sel=3'b011; #10

```

```

sel=3'b100; #10
sel=3'b101; #10
sel=3'b110; #10
sel=3'b111; #10
in=8'b11101000;
sel=3'b000; #10
sel=3'b010; #10
sel=3'b001; #10
sel=3'b011; #10
sel=3'b100; #10
sel=3'b101; #10
sel=3'b110; #10
sel=3'b111; #10
$finish;
end
endmodule

```



### 13.DeMultiplexer(1\*8)

#### Verilog Code:

```

module eight_demux(in,en,sel,out );
input in,en;
input[2:0]sel;
output reg [7:0]out;
always @(*)
begin
out=8'b00000000;
if(en)

```

```

begin
case(sel)
3'b000: out[0]=in;
3'b001: out[1]=in;
3'b010: out[2]=in;
3'b011: out[3]=in;
3'b100: out[4]=in;
3'b101: out[5]=in;
3'b110: out[6]=in;
3'b111: out[7]=in;
default:out=8'b00000000;
endcase
end
else
out=8'b00000000;
end
endmodule

```


### **TestBench:**

```

module tb5(out );
reg in,en;
reg[2:0]sel;
output [7:0] out;
eight_demux dut(in,en,sel,out);
initial
begin
in=1;en=1;
sel=3'b000; #10
sel=3'b001; #10
sel=3'b010; #10
sel=3'b011; #10
sel=3'b100; #10
sel=3'b101; #10
sel=3'b110; #10
sel=3'b111; #10
en=0; #10
en=1; #10
in=0; #10
in=1; #10
$finish;
end
endmodule

```



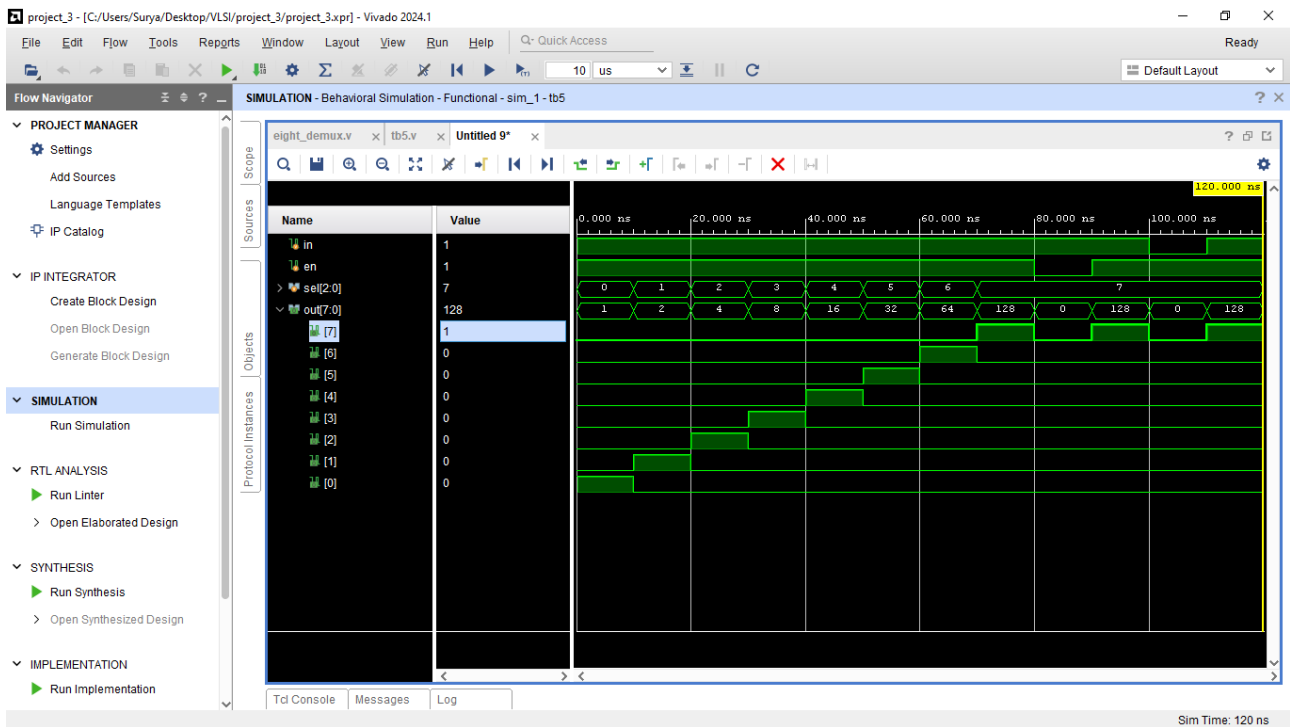

## 14.Encoder

### Verilog Code:


```

module encoder(in,out);
input[7:0] in;
output reg[2:0] out;
always @(*)
begin
out=3'b000;
case(in)
8'b00000000: out=3'b000;
8'b00000001: out=3'b000;
8'b00000010: out=3'b001;
8'b00000100: out=3'b010;
8'b00001000: out=3'b011;
8'b00010000: out=3'b100;
8'b00100000: out=3'b101;
8'b01000000: out=3'b110;
8'b10000000: out=3'b111;
default: out=3'b000;
endcase
end
endmodule

```
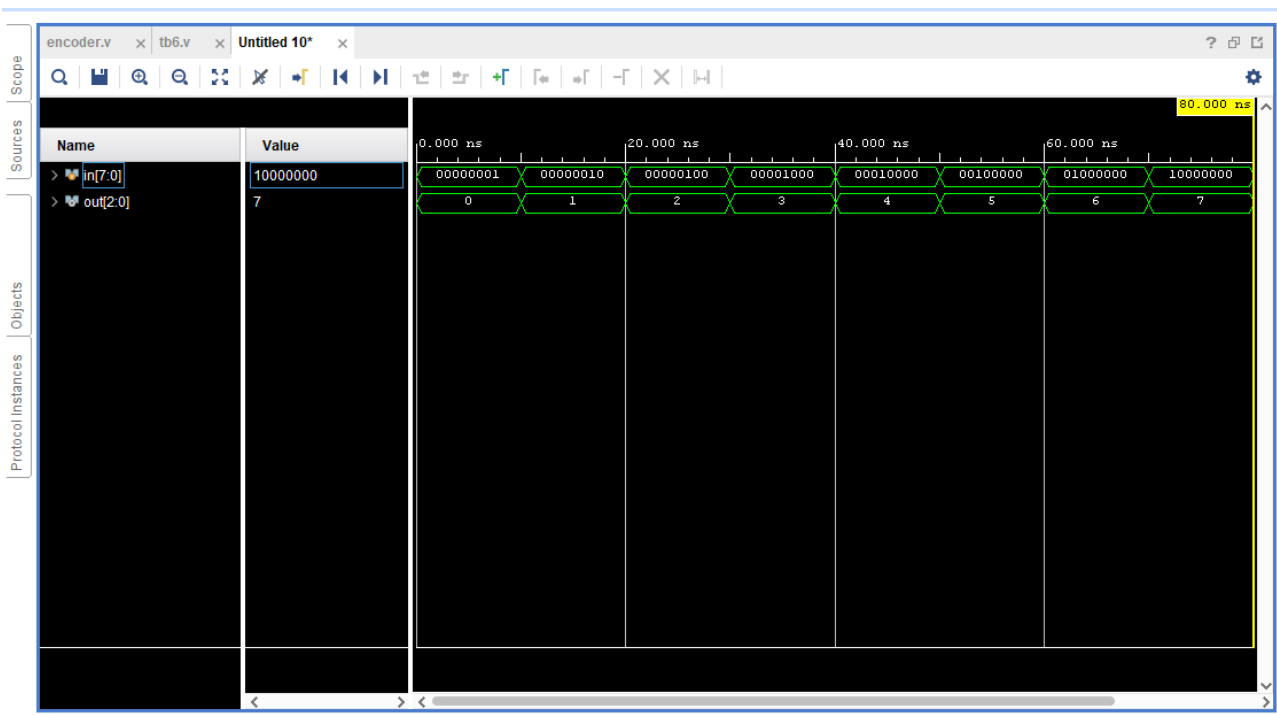
### TestBench:

```
module tb6( );
reg [7:0] in;
wire [2:0] out;
encoder dut(in,out);
initial
begin
in=8'b00000001; #10
in=8'b00000010; #10
in=8'b00000100; #10
in=8'b00001000; #10
in=8'b00010000; #10
in=8'b00100000; #10
in=8'b01000000; #10
in=8'b10000000; #10
$finish;
end
endmodule
```



## 15. Priority Encoder


### Verilog Code:

```
module priority_encoder(in,out );
input [3:0] in;
output [1:0] out;
assign out[1]= in[2]|in[3];
```

```
assign out[0]=in[3]|((~in[2])&in[0]);
endmodule
```
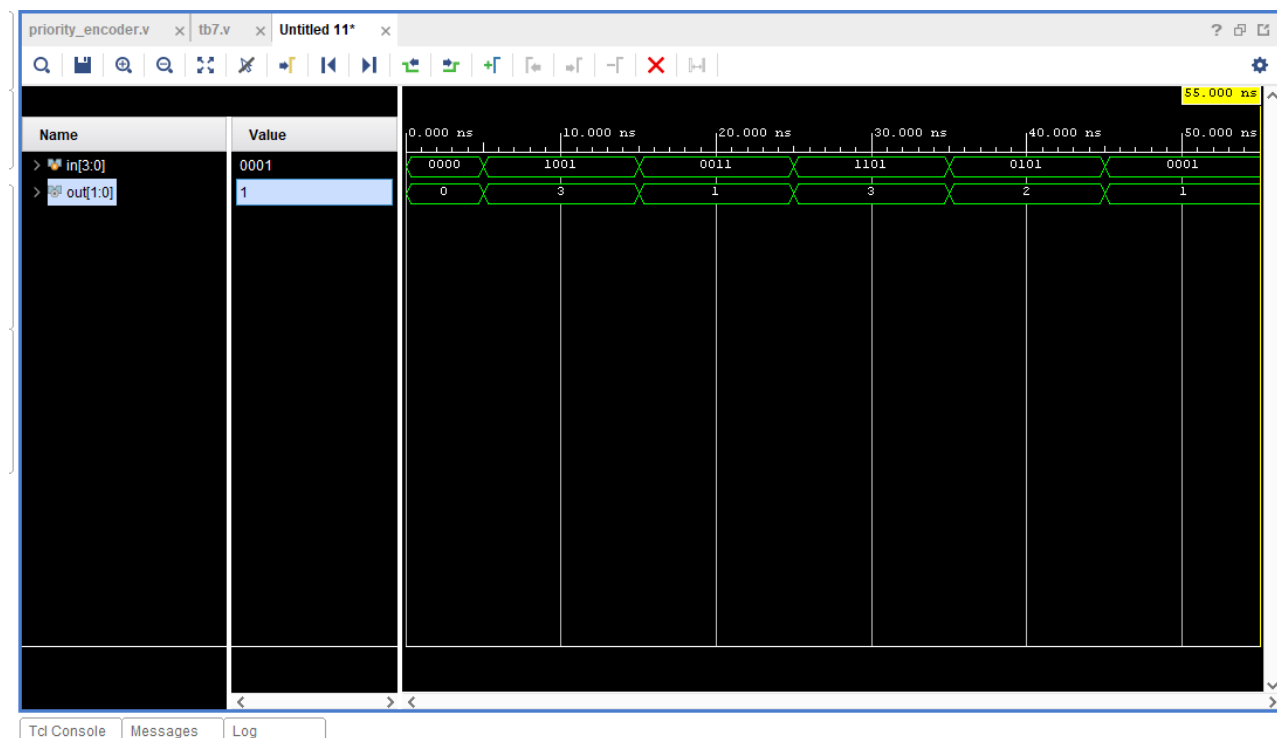
### TestBench:

```
module tb7();
reg [3:0] in;
wire [1:0] out;
priority_encoder uut(in,out);
initial
begin
in=4'b0000; #5
in=4'b1001; #10
in=4'b0011; #10
in=4'b1101; #10
in=4'b0101; #10
in=4'b0001; #10
$finish;
end
endmodule
```



## 16. 4-bit Comparator

### Verilog Code:

```
module comparator_4bit(a,b,lt,eq,gt );
input [3:0] a,b;
```

```

output lt,eq,gt;
assign lt=(a<b);
assign eq=(a==b);
assign gt=(a>b);
endmodule


```

### TestBench:

```

module tb_8();
reg [3:0] a,b;
wire lt,eq,gt;
comparator_4bit uut(a,b,lt,eq,gt);
initial
begin
a=4'b0010; b=4'b1001; #10
a=4'b1110; b=4'b1001; #10
a=4'b0010; b=4'b1001; #10
a=4'b0000; b=4'b0000; #10
a=4'b1010; b=4'b1010; #10
a=4'b1101; b=4'b1001; #10
$finish;
end
endmodule

```

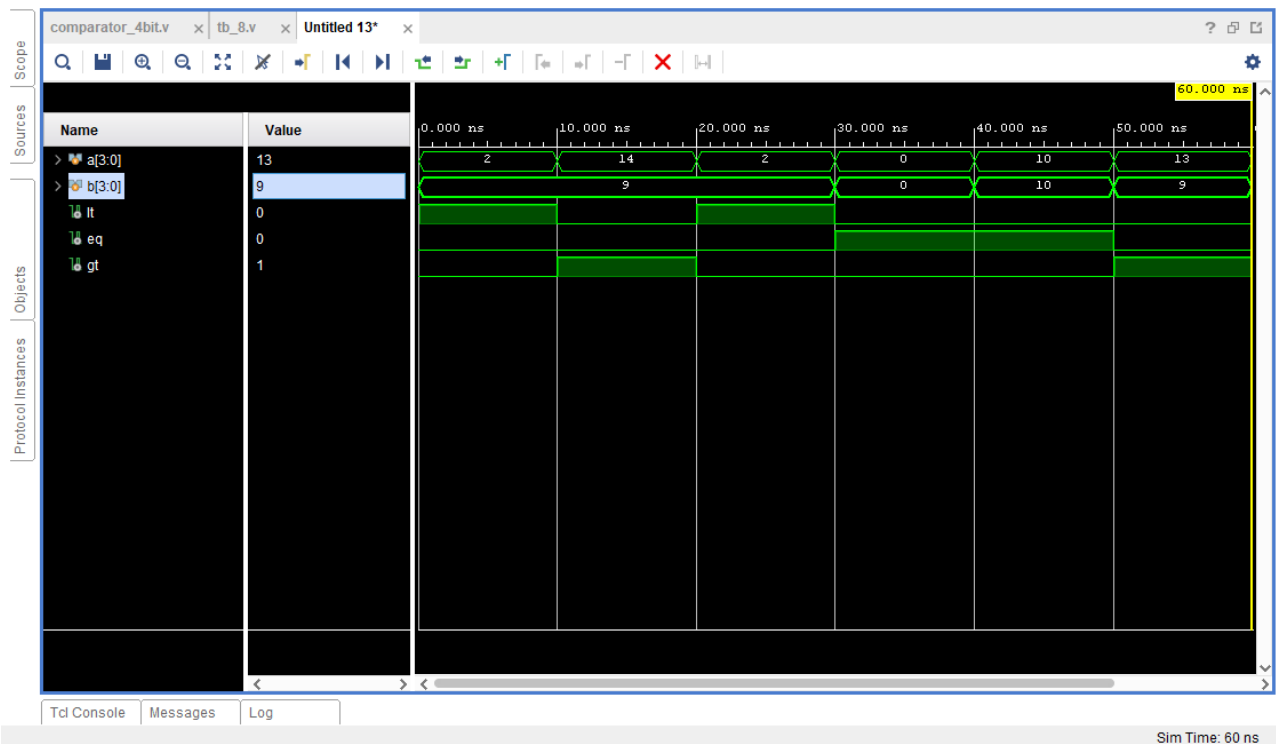


## 17.Decimal-BCD Encoder

### VerilogCode:

```
module decimal_bcd_encoder(in,out );
input[9:0]in;
output [3:0] out;
assign out[3]=in[8]|in[9];
assign out[2]=in[4]|in[5]|in[6]|in[7];
assign out[1]=in[2]|in[3]|in[6]|in[7];
assign out[0]=in[1]|in[3]|in[5]|in[7]|in[9];
endmodule
```
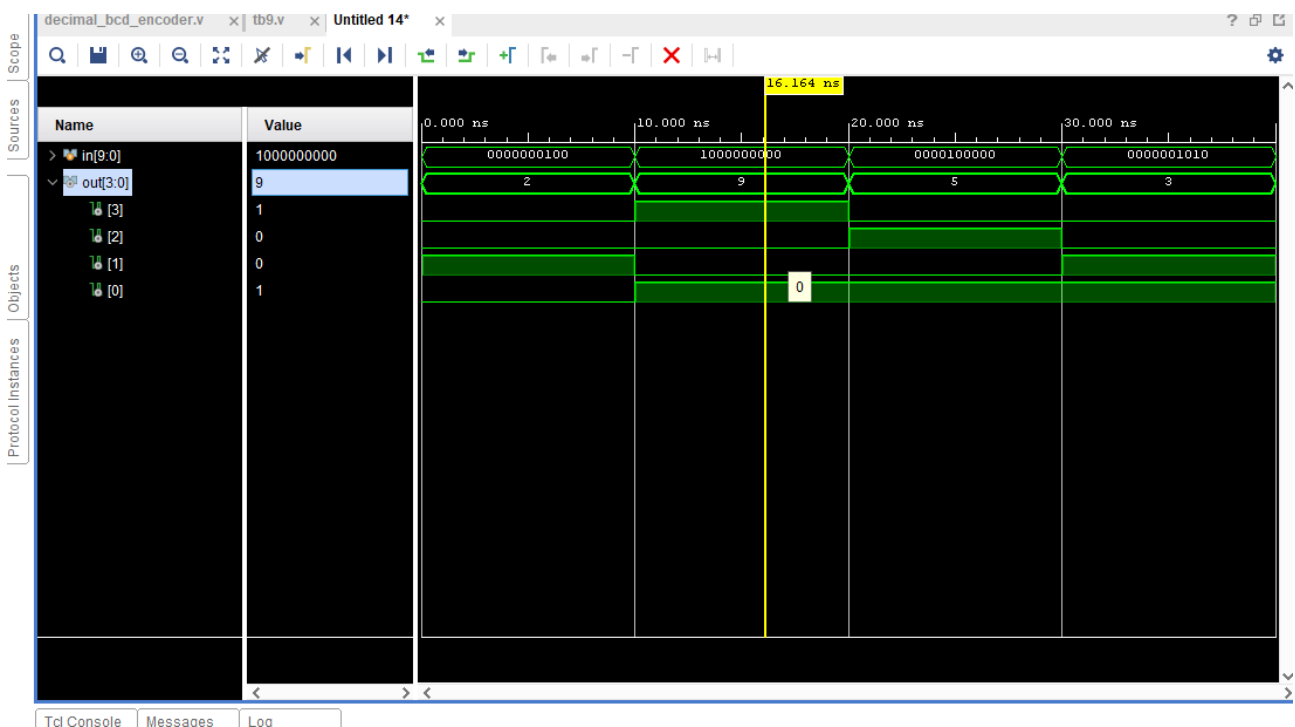
### TestBench:

```
module tb9( );
reg [9:0] in;
wire [3:0] out;
decimal_bcd_encoder uut (in,out);
initial
begin
in=10'b00000000100; #10
in=10'b10000000000; #10
in=10'b00001000000; #10
in=10'b0000001010; #10
$finish;
end
endmodule
```




## 18. Octal-Binary Encoder

### Verilog Code:

```
module octal_binary_encoder(in,out);
input[7:0]in;
output[2:0] out;
assign out[2]=in[4]|in[5]|in[6]|in[7];
assign out[1]=in[2]|in[3]|in[6]|in[7];
assign out[0]=in[1]|in[3]|in[5]|in[7];
endmodule
```
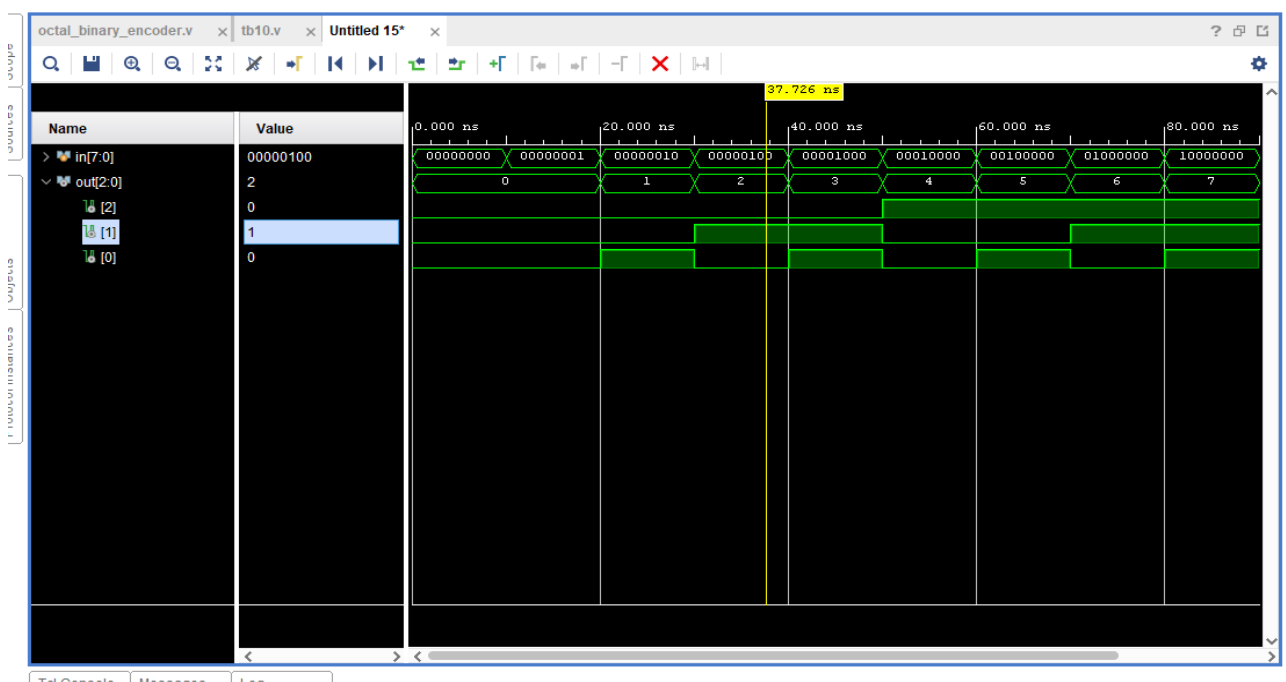
### TestBench:

```
module tb10();
reg [7:0] in;
wire [2:0] out;
octal_binary_encoder uut(in,out);
initial
begin
in=8'b00000000; #10
in=8'b00000001; #10
in=8'b00000010; #10
in=8'b00000100; #10
in=8'b00001000; #10
in=8'b00010000; #10
in=8'b00100000; #10
in=8'b01000000; #10
in=8'b10000000; #10
$finish;
end
endmodule
```




## 19.Hexadecimal-Binary Encoder

### Verilog Code:

```
module hexadecimal_binary(in,out );
input [15:0] in;
output[3:0] out;
assign out[3]=in[8]|in[9]|in[10]|in[11]|in[12]|in[13]|in[14]|in[15];
assign out[2]=in[4]|in[5]|in[6]|in[7]|in[12]|in[13]|in[14]|in[15];
assign out[1]=in[2]|in[3]|in[6]|in[7]|in[10]|in[11]|in[14]|in[15];
assign out[0]=in[1]|in[3]|in[5]|in[7]|in[9]|in[11]|in[13]|in[15];
endmodule
```
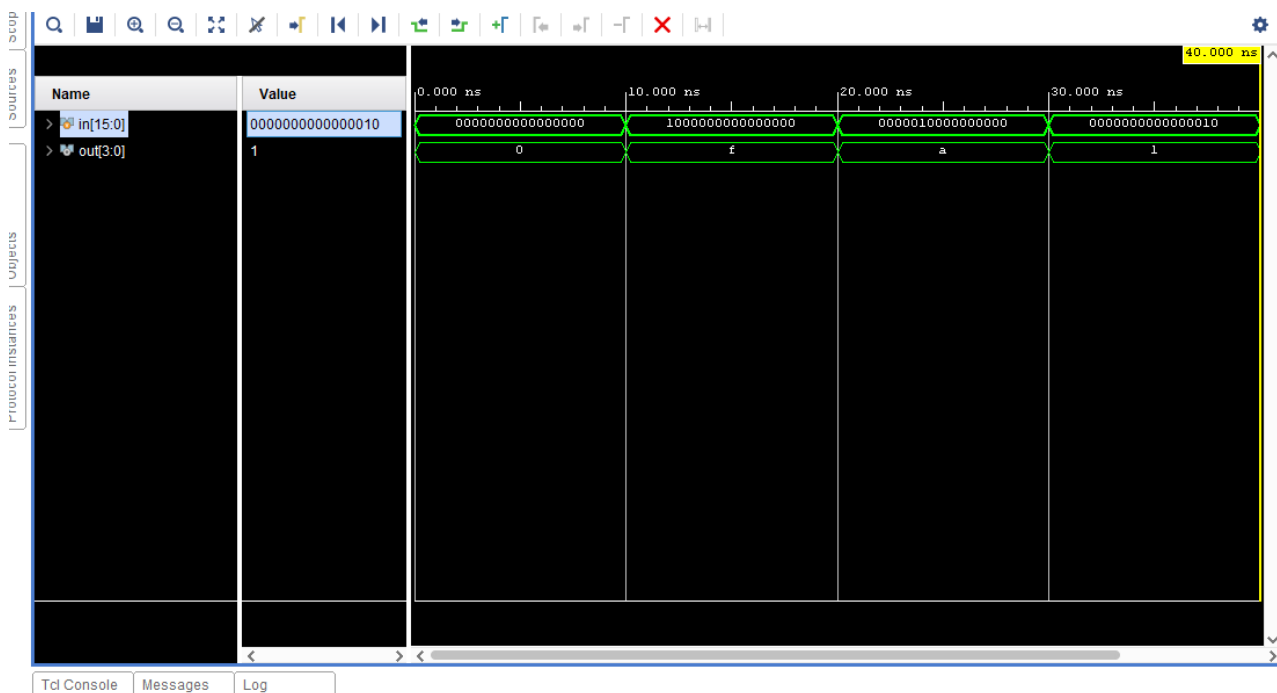
### TestBench:

```
module tb11();
reg [15:0] in;
wire [3:0]out;
hexadecimal_binary uut(in,out);
initial
begin
in=16'h0000; #10
in=16'h8000; #10
in=16'h0400; #10
in=16'h0002; #10
$finish;
end
endmodule
```




## 20.Binary-Gray Converter

### Verilog Code:

```
module binary_gray_conv(bin,gray);
input[3:0] bin;
output[3:0]gray;
assign gray[3]=bin[3];
assign gray[2]=bin[3]^bin[2];
assign gray[1]=bin[2]^bin[1];
assign gray[0]=bin[1]^bin[0];
endmodule
```
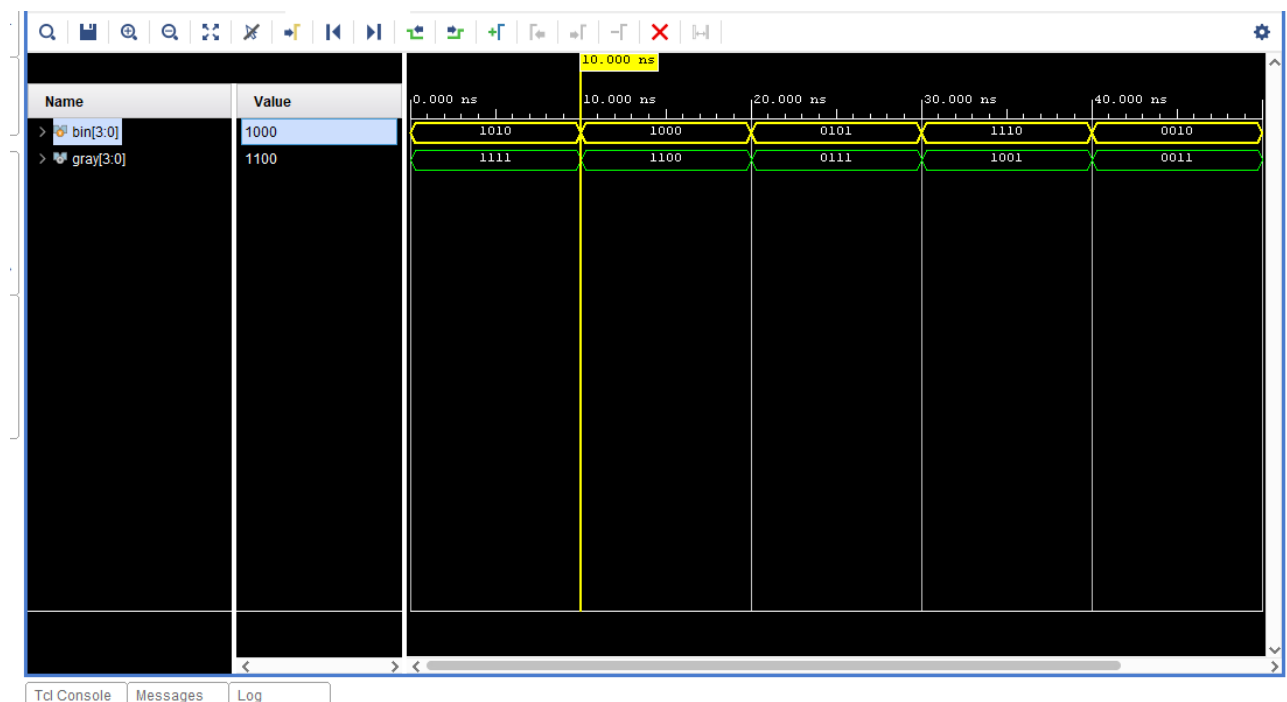
### TestBench:

```
module tb1();
reg[3:0]bin;
wire[3:0]gray;
binary_gray_conv uut(bin,gray);
initial
begin
bin=4'b1010; #10
bin=4'b1000; #10
bin=4'b0101; #10
bin=4'b1110; #10
bin=4'b0010; #10
$finish;
end
endmodule
```






## 21.Gray-Binary Converter

### Verilog Code:

```
module gray_binary_conv(gray,bin);
input[3:0] gray;
output[3:0] bin;
assign bin[3]= gray[3];
assign bin[2]=gray[2]^bin[3];
assign bin[1]=gray[1]^bin[2];
assign bin[0]=gray[0]^bin[1];
endmodule
```
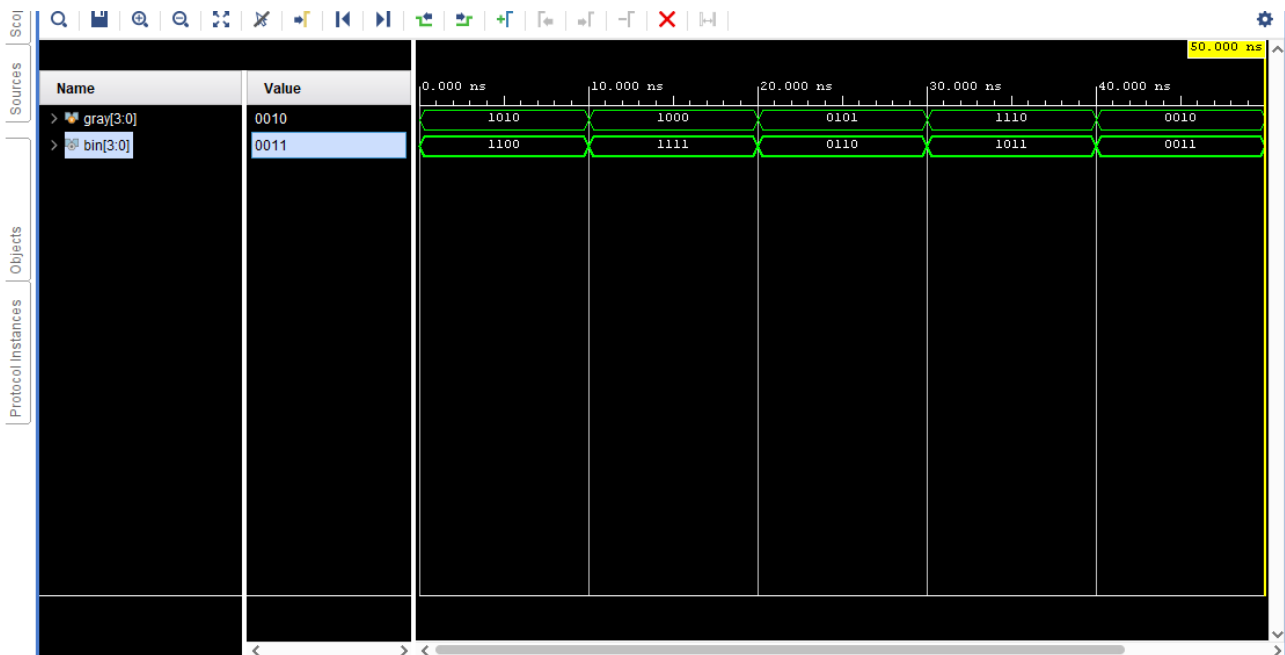
### TestBench:

```
module tb2( );
reg[3:0]gray;
wire[3:0]bin;
gray_binary_conv uut(gray,bin);
initial
begin
gray=4'b1010; #10
gray=4'b1000; #10
gray=4'b0101; #10
gray=4'b1110; #10
gray=4'b0010; #10
$finish;
end
endmodule
```




## 22. Even Parity Generator

### Verilog Code:

```
module even_parity_gen(in,p );
input [3:0]in;
output p;
assign p=in[3]^in[2]^in[1]^in[0];
endmodule
```
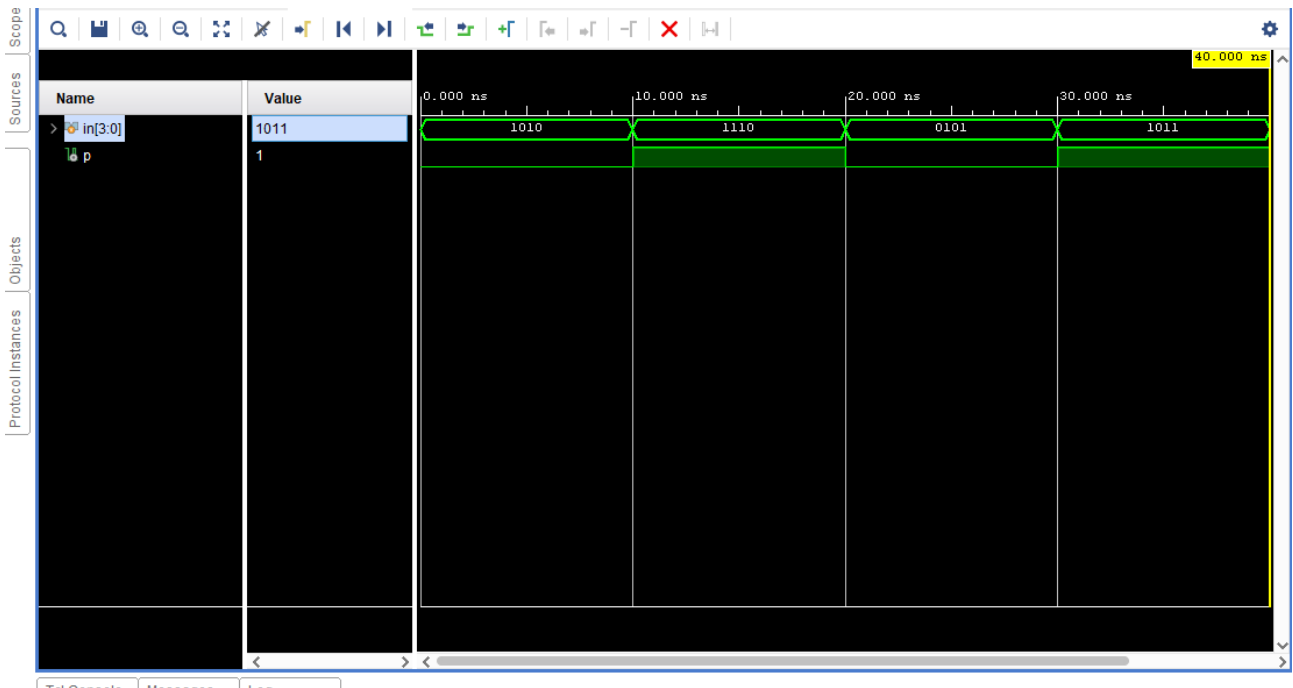
### TestBench:

```
module tb3();
reg[3:0]in;
wire p;
even_parity_gen uut(.p(p),.in(in));
initial
begin
in=4'b1010; #10
in=4'b1110; #10
in=4'b0101; #10
in=4'b1011; #10
$finish;
end
endmodule
```




## 23.Odd Parity Generator

### Verilog Code:

```
module odd_parity_gen(in,p);  
input[3:0]in;  
output p;  
assign p=~(in[3]^in[2]^in[1])^in[0];  
endmodule
```
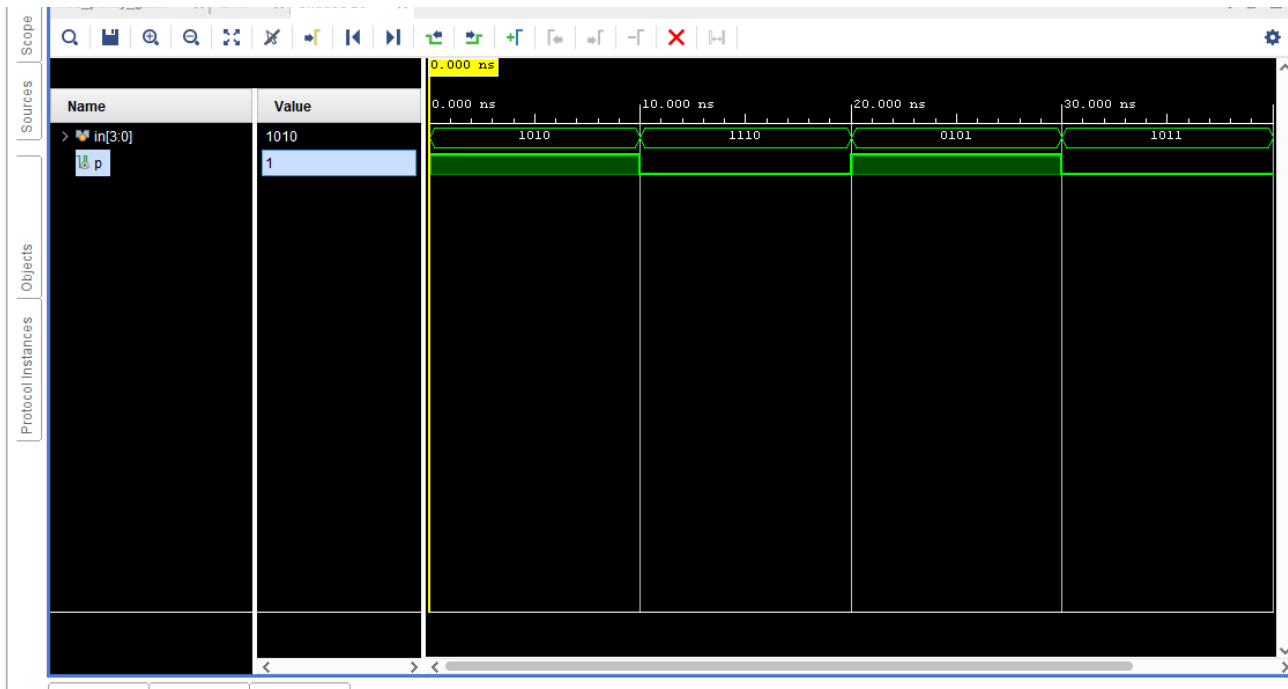
### TestBench:

```
module tb4();  
reg[3:0]in;  
wire p;  
odd_parity_gen uut(.p(p),.in(in));  
initial  
begin  
in=4'b1010; #10  
in=4'b1110; #10  
in=4'b0101; #10  
in=4'b1011; #10  
$finish;  
end  
endmodule
```




## 24. Even Parity Checker

### Verilog Code:

```
module even_parity_check(in,p,error );
input[3:0]in;
input p;
output error;
assign error=in[3]^in[2]^in[1]^in[0]^p;
endmodule
```
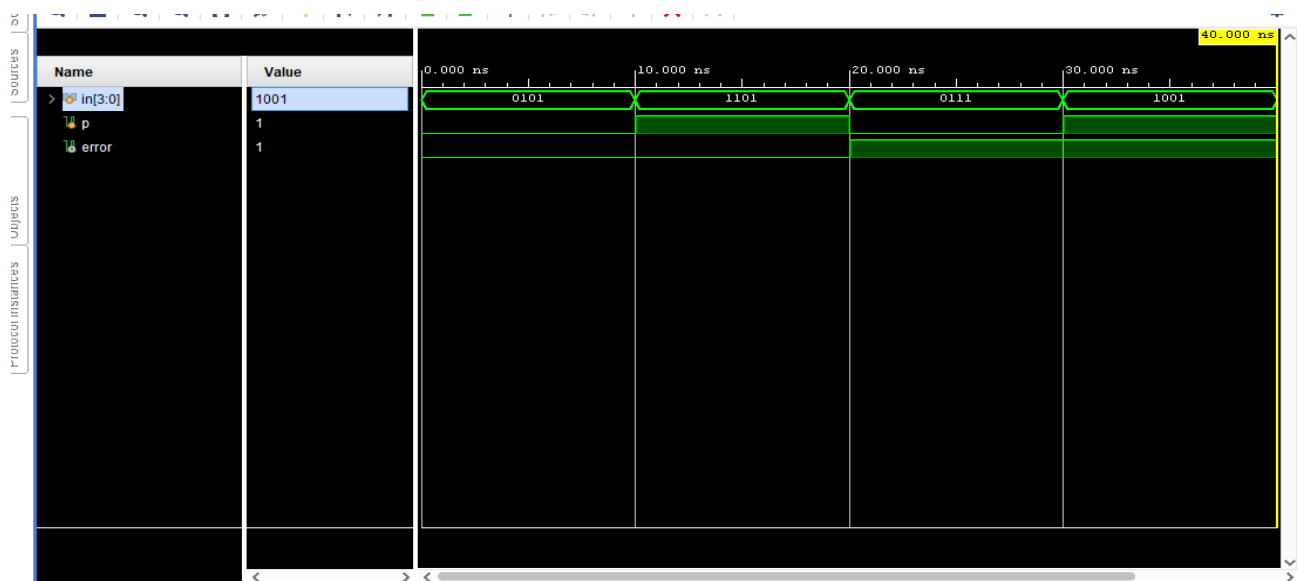
### TestBench:

```
module tb5();
reg[3:0]in;
reg p;
wire error;
even_parity_check uut(in,p,error);
initial
begin
in=4'b0101; p=1'b0; #10
in=4'b1101; p=1'b1; #10
in=4'b0111; p=1'b0; #10
in=4'b1001; p=1'b1; #10
$finish;
end
endmodule
```




## 25.Odd Parity Checker

### Verilog Code:

```
module odd_parity_check(in,p,error );
input[3:0]in;
input p;
output error;
assign error=~(in[3]^in[2]^in[1]^in[0])^p;
endmodule
```
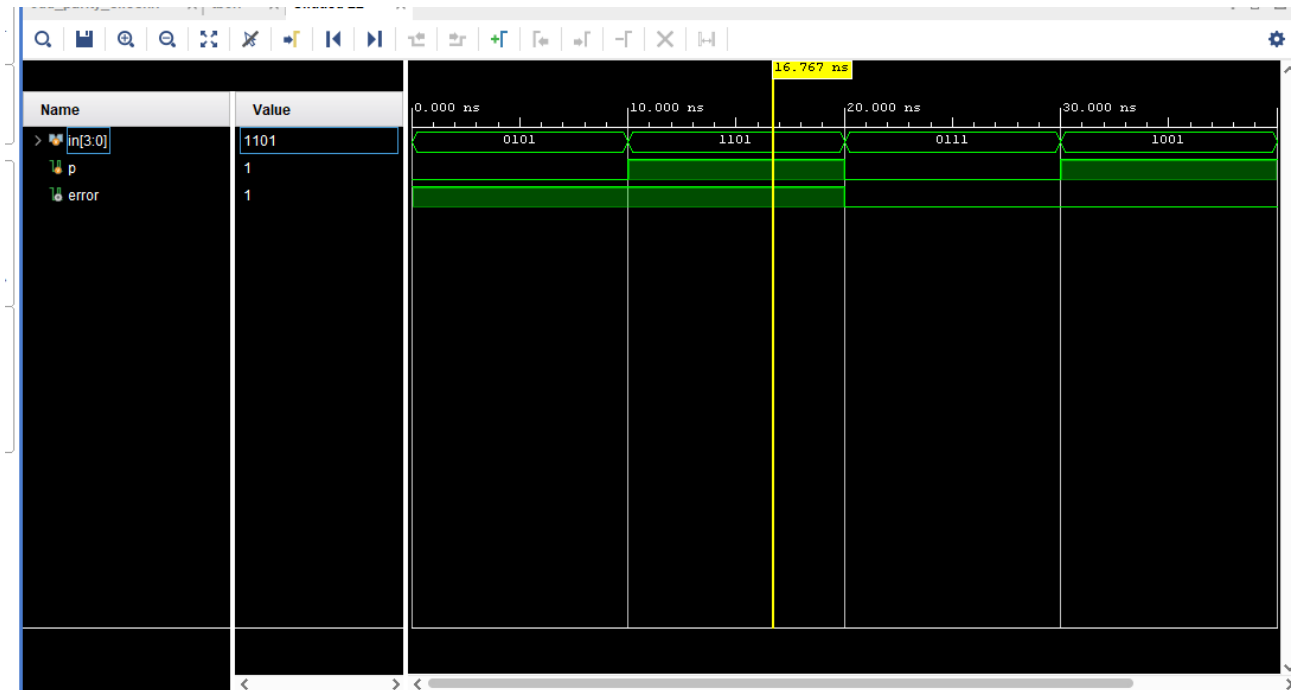
### TestBench:

```
module tb6();
reg[3:0]in;
reg p;
wire error;
odd_parity_check uut(in,p,error);
initial
begin
in=4'b0101; p=1'b0; #10
in=4'b1101; p=1'b1; #10
in=4'b0111; p=1'b0; #10
in=4'b1001; p=1'b1; #10
$finish;
end
endmodule
```




## 26.Binary-Seven Segment Display Converter

### Verilog Code:

```
module bcd_sevensegment_conv(D,a,b,c,d,e,f,g );
input[3:0]D;
output reg a,b,c,d,e,f,g;
always @(*)
begin
case(D)
4'b0000: {a,b,c,d,e,f,g} = 7'b1111110;
4'b0001: {a,b,c,d,e,f,g} = 7'b0110000;
4'b0010: {a,b,c,d,e,f,g} = 7'b1101101;
4'b0011: {a,b,c,d,e,f,g} = 7'b1111001;
4'b0100: {a,b,c,d,e,f,g} = 7'b0110011;
4'b0101: {a,b,c,d,e,f,g} = 7'b1011011;
4'b0110: {a,b,c,d,e,f,g} = 7'b1011111;
4'b0111: {a,b,c,d,e,f,g} = 7'b1110000;
4'b1000: {a,b,c,d,e,f,g} = 7'b1111111;
4'b1001: {a,b,c,d,e,f,g} = 7'b1111011;
default: {a,b,c,d,e,f,g} = 7'b0000000;
endcase
end
endmodule
```
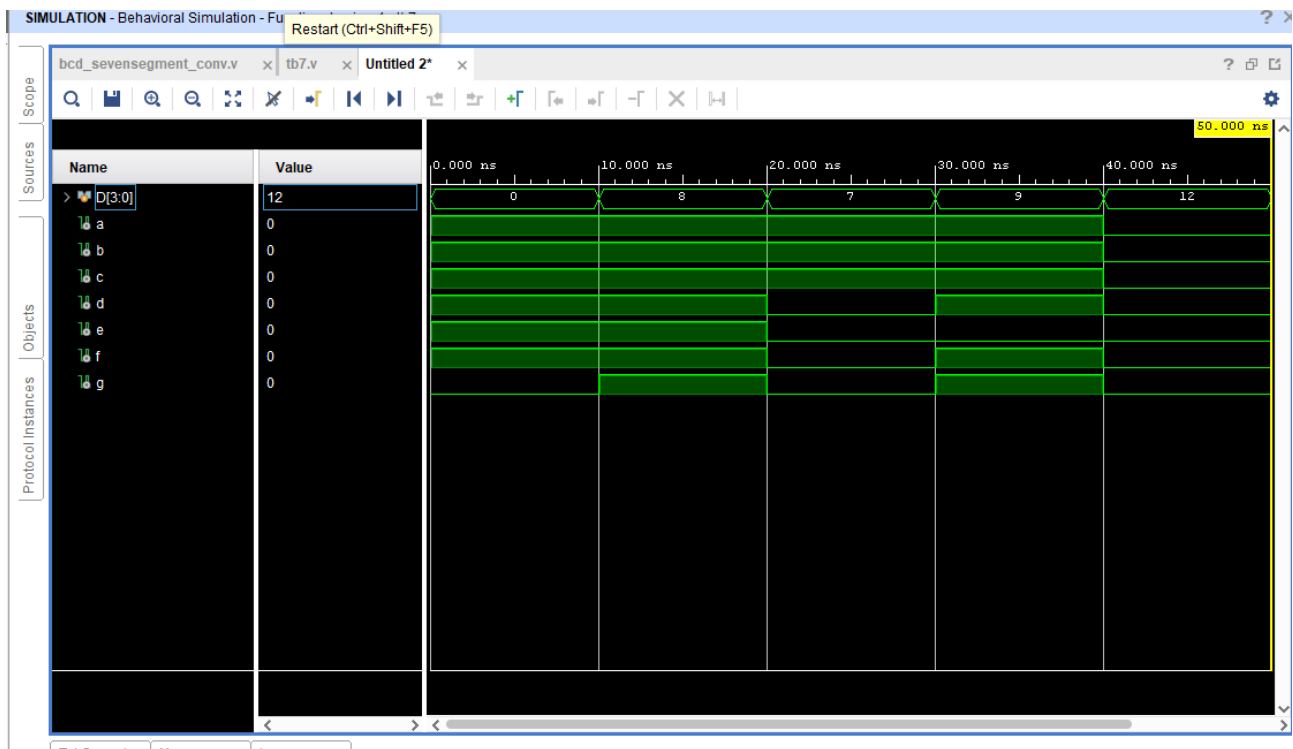
### TestBench:

```
module tb7();
reg[3:0]D;
wire a,b,c,d,e,f,g;
bcd_sevensegment_conv uut(D,a,b,c,d,e,f,g);
initial
begin
D=4'b0000; #10
D=4'b1000; #10
D=4'b0111; #10
D=4'b1001; #10
D=4'b1100; #10
$finish;
end
endmodule
```



## 27. Carry Look Ahead Adder

### Verilog Code:

```

module carry_look_ahead_adder(
    input [3:0] A, B,
    input Cin,
    output [3:0] S,
    output Cout,
    output [4:0] out);
    wire G[3:0], P[3:0];
    wire C[4:0];

    assign G[0] = A[0] & B[0];
    assign G[1] = A[1] & B[1];
    assign G[2] = A[2] & B[2];
    assign G[3] = A[3] & B[3];

    assign P[0] = A[0] | B[0];
    assign P[1] = A[1] | B[1];
    assign P[2] = A[2] | B[2];
    assign P[3] = A[3] | B[3];

    assign C[0] = Cin;
    assign C[1] = G[0] | (P[0] & Cin);
    assign C[2] = G[1] | (P[1] & (G[0] | (P[0] & Cin)));
    assign C[3] = G[2] | (P[2] & (G[1] | (P[1] & (G[0] | (P[0] & Cin)))));

```

```
assign Cout = G[3] | (P[3] & (G[2] | (P[2] & (G[1] | (P[1] & (G[0] | (P[0] & Cin))))));
```

```
assign S[0] = A[0] ^ B[0] ^ C[0];
```

```
assign S[1] = A[1] ^ B[1] ^ C[1];
```

```
assign S[2] = A[2] ^ B[2] ^ C[2];
```

```
assign S[3] = A[3] ^ B[3] ^ C[3];
```

```
assign out={Cout,S};
```

```
endmodule
```

## TestBench:

```
module tb8();
```

```
reg[3:0] A, B;
```

```
reg Cin;
```

```
wire[3:0] S;
```

```
wire Cout;
```

```
wire [4:0]out;
```

```
carry_look_ahead_adder uut(A,B,Cin,S,Cout,out);
```

```
initial
```

```
begin
```

```
A=4'b1000; B=4'b1000; Cin=1'b1; #10
```

```
A=4'b1100; B=4'b0010; Cin=1'b1; #10
```

```
A=4'b0100; B=4'b0111; Cin=1'b0; #10
```


```
A=4'b1111; B=4'b1100; Cin=1'b1; #10
```

```
A=4'b1111; B=4'b1111; Cin=1'b1; #10
```

```
$finish;
```

```
end
```

```
endmodule
```

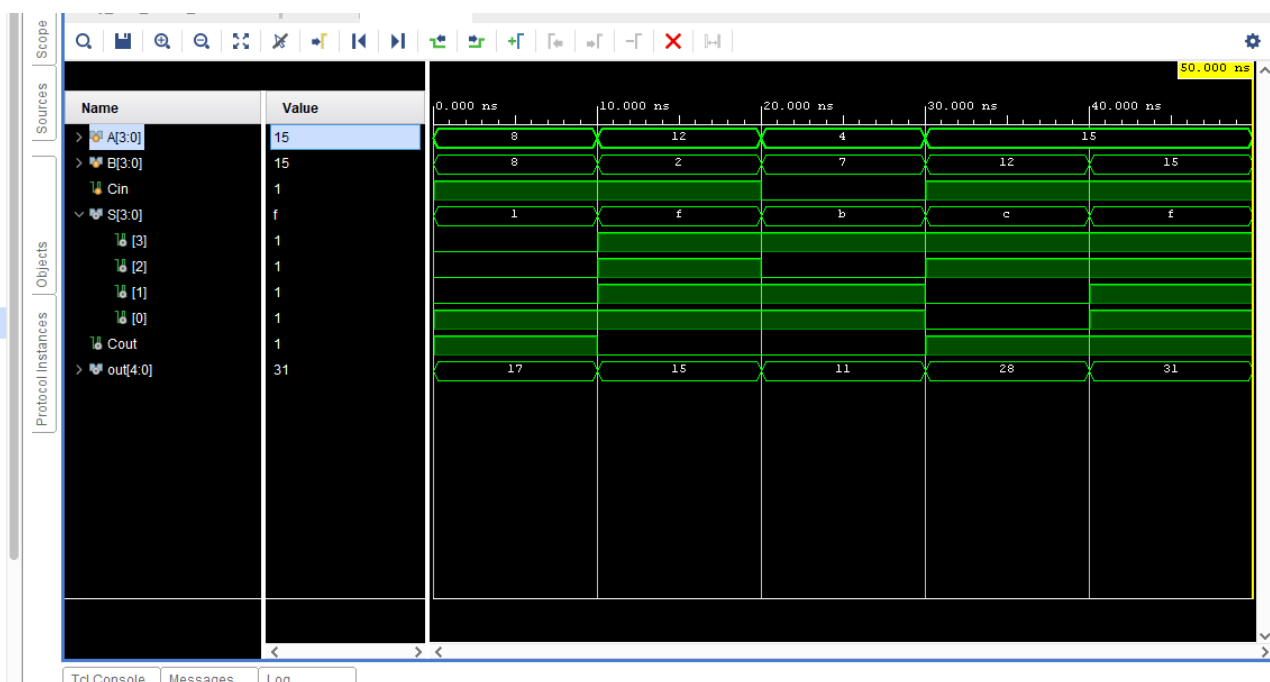




## 28.BCD Adder

### Verilog Code:

```
module bcd_addition(a,b,cin,sum,cout );
input[3:0]a,b;
input cin;
output[3:0]sum;
output cout;
reg cout_temp;reg[4:0]sum_temp;
always @(*)
begin
sum_temp=a+b+cin;
if(sum_temp>9)
begin
sum_temp=sum_temp+6;
cout_temp=1;
end
else
sum_temp=sum_temp[3:0];
cout_temp=sum_temp[4];
end
assign sum=sum_temp;
assign cout=cout_temp;
endmodule
```
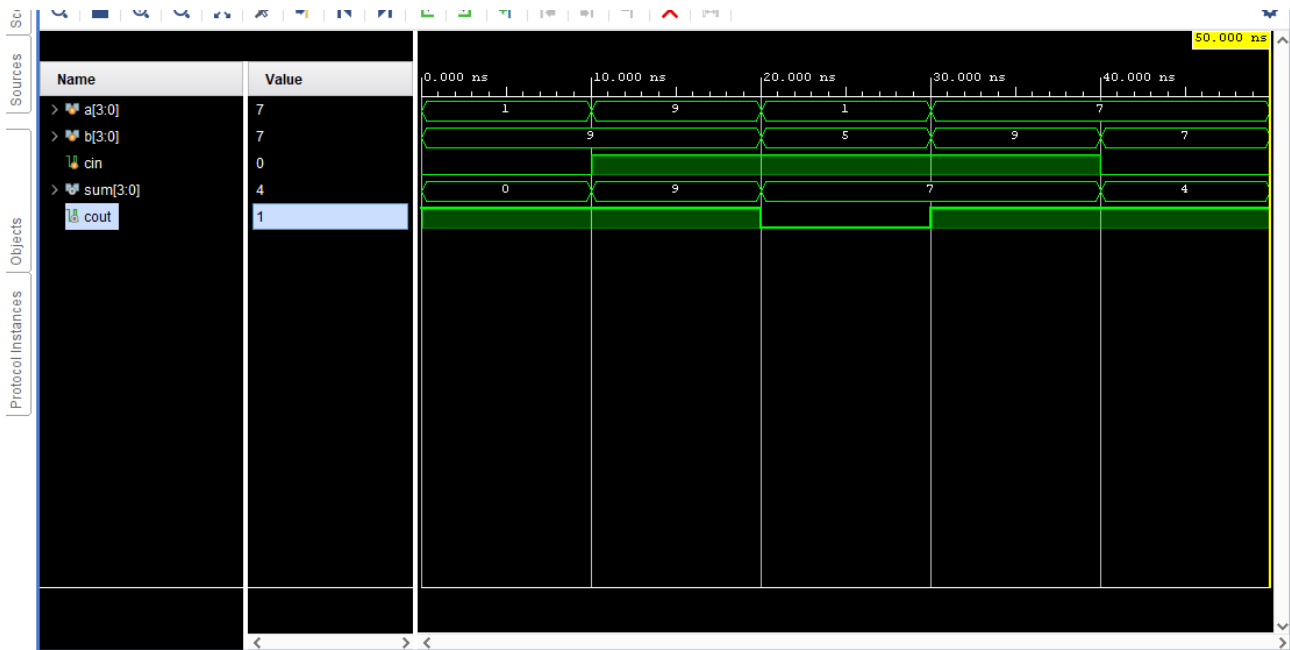
### TestBench:

```
module tb9( );
reg [3:0]a,b;
reg cin;wire[3:0]sum;wire cout;
bcd_addition uut(a,b,cin,sum,cout);
initial
begin
a=4'b0001; b=4'b1001; cin=0; #10;
a=4'b1001; b=4'b1001; cin=1; #10;
a=4'b0001; b=4'b0101; cin=1; #10;
a=4'b0111; b=4'b1001; cin=1; #10;
a=4'b0111; b=4'b0111; cin=0; #10;
$finish;
end
endmodule
```



## 29.BCD-Excess\_3 Converter

### Verilog Code:

```
module bcd_x3_conv(b,x);
input[3:0]b;
output[3:0]x;
assign x[3]=b[3]|(b[2]&b[1])|(b[2]&b[0]);
assign x[2]=(~b[2]&b[0])|(~b[2]&b[1])|(b[2]&~b[1]&~b[0]);
assign x[1]=(b[1]&b[0])|(~b[1]&~b[0]);
assign x[0]=~b[0];
endmodule
```


### TestBench:

```
module tb1( );
reg[3:0]b;
wire[3:0]x;
bcd_x3_conv uut(b,x);
initial
begin
b=4'b0000; #10
b=4'b0001; #10
b=4'b0010; #10
b=4'b0011; #10
b=4'b0100; #10
b=4'b0101; #10
b=4'b0110; #10
b=4'b0111; #10
b=4'b1000; #10
end
```

```

b=4'b1001; #10
$finish;
end
endmodule

```

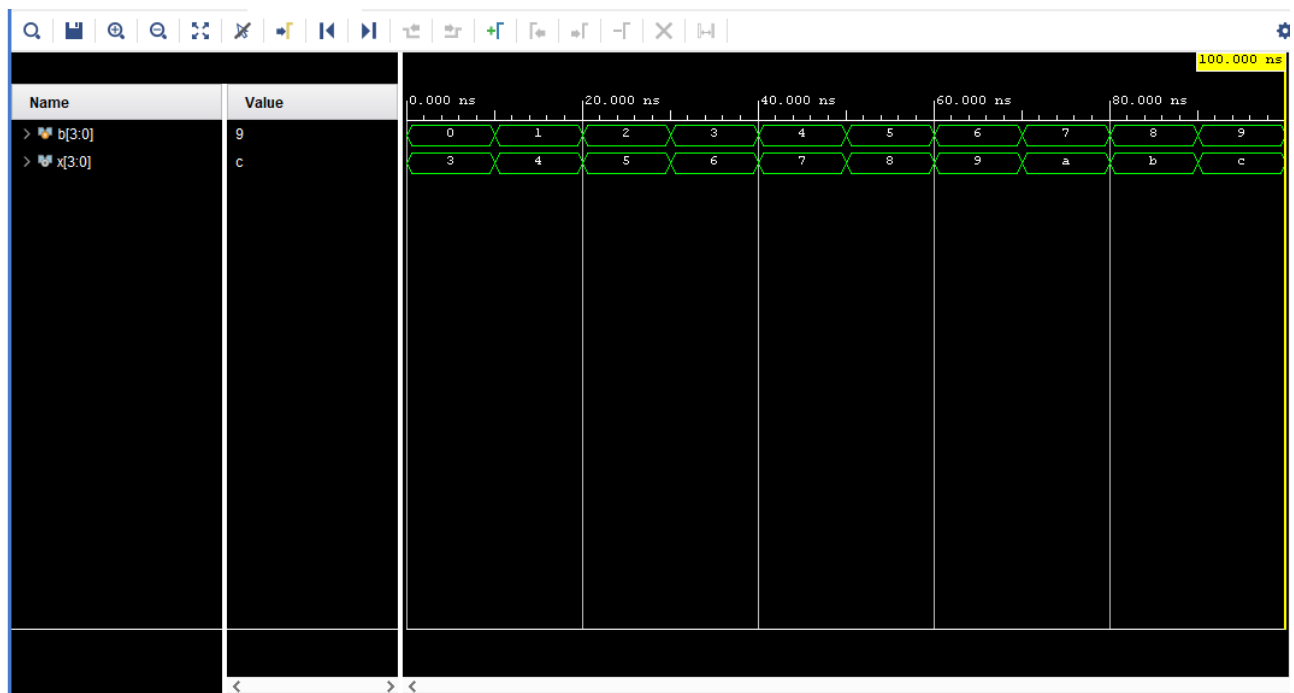

## 30. Carry Save Adder

### Verilog Code:

```

module full_addr(a,b,c,sum,carry);
input a,b,c; output sum,carry;
assign sum=a^b^c;
assign carry=(a&b)|(b&c)|(a&c);
endmodule


module carry_save_adder(a,b,c,sum,cout,out );
input[3:0]a,b,c;
output [4:0] sum;output cout;
output[5:0]out;
wire [3:0]sum_temp,cout_temp,co;
full_addr fa1(a[0],b[0],c[0],sum_temp[0],cout_temp[0]);
full_addr fa2(a[1],b[1],c[1],sum_temp[1],cout_temp[1]);
full_addr fa3(a[2],b[2],c[2],sum_temp[2],cout_temp[2]);
full_addr fa4(a[3],b[3],c[3],sum_temp[3],cout_temp[3]);
full_addr fa5(sum_temp[1],cout_temp[0],1'b0,sum[1],co[0]);
full_addr fa6(sum_temp[2],cout_temp[1],co[0],sum[2],co[1]);
full_addr fa7(sum_temp[3],cout_temp[2],co[1],sum[3],co[2]);
full_addr fa8(1'b0,cout_temp[3],co[2],sum[4],cout);
assign sum[0]=sum_temp[0];

```

```
assign out={cout,sum};
endmodule
```
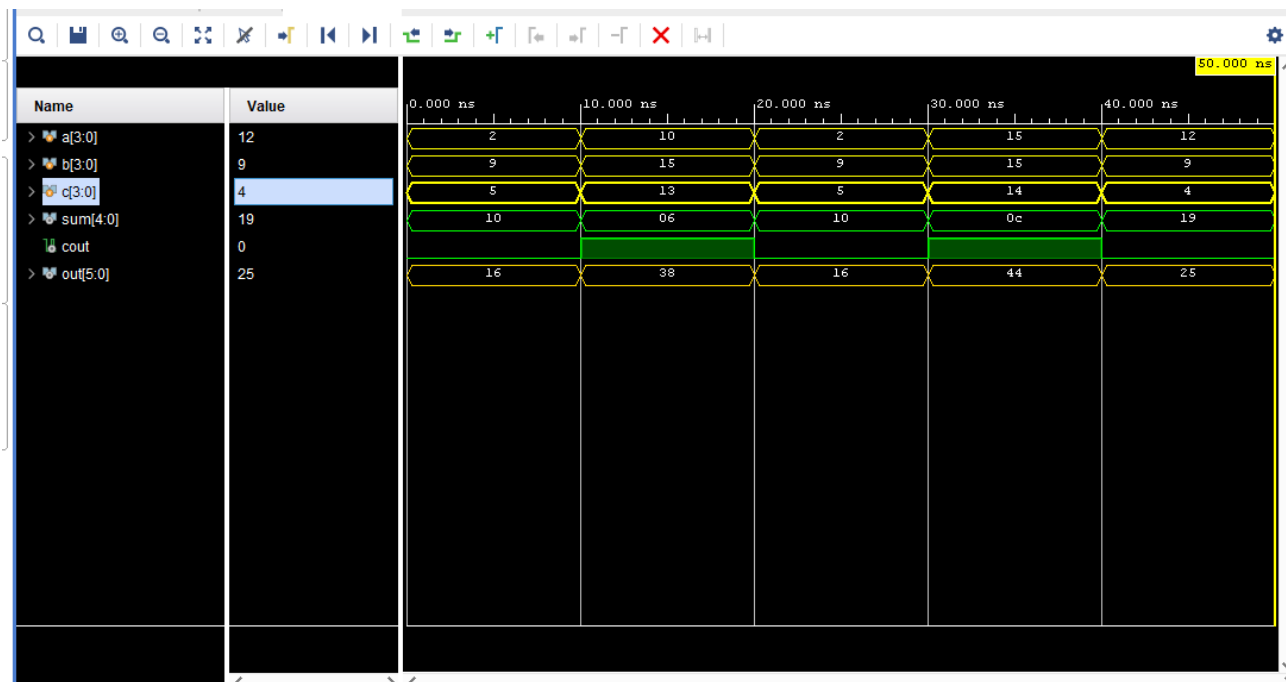
### TestBench:

```
module tb2();
reg[3:0]a,b,c;
wire[4:0]sum; wire cout; wire[5:0]out;
carry_save_adder uut(a,b,c,sum,cout,out);
initial
begin
a=4'b0010; b=4'b1001; c=4'b0101; #10
a=4'b1010; b=4'b1111; c=4'b1101; #10
a=4'b0010; b=4'b1001; c=4'b0101; #10
a=4'b1111; b=4'b1111; c=4'b1110; #10
a=4'b1100; b=4'b1001; c=4'b0100; #10
$finish;
end
endmodule
```



## 31. Squares of 3bit numbers

### Verilog Code:

```
module squares_3bit(in,out );
input[2:0]in;output[5:0]out;
assign out[5]=in[2]&in[1];
assign out[4]=(in[2]&~in[1])|(in[0]&in[2]);
assign out[3]=in[0]&(in[1]^in[2]);
assign out[2]=in[1]&~in[0];
```

```

assign out[1]=1'b0;
assign out[0]=in[0];
endmodule


```

### TestBench:

```

module tb3( );
reg[2:0]in;wire[5:0]out;
squares_3bit dut(in,out);
integer count;
initial
begin
in=3'b000;#10
in=3'b001;#10
in=3'b010;#10
in=3'b011;#10
in=3'b100;#10
in=3'b101;#10
in=3'b110;#10
in=3'b111;#10
$finish;
end
endmodule

```

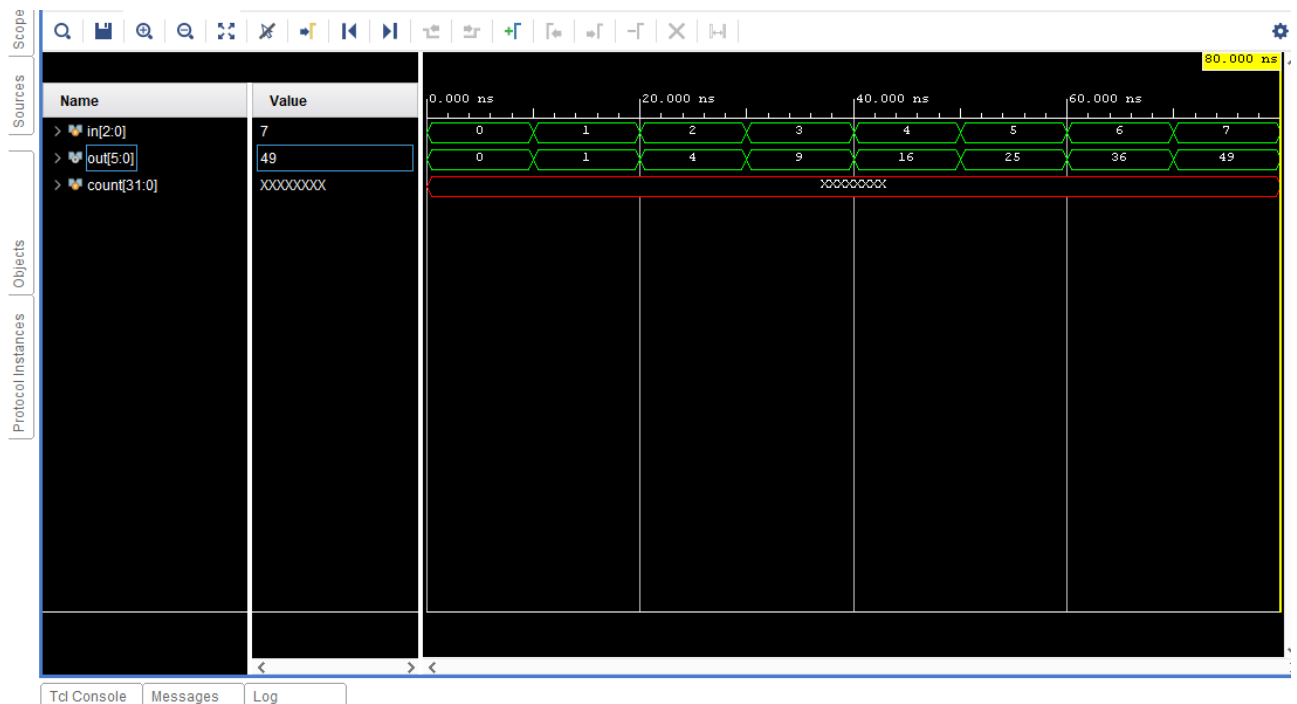


## 32.Tristate Buffer

### Verilog Code:

```
module tristate_buffer(in,en,out);  
input in,en;output out;  
assign out=en?in:1'bz;  
endmodule
```
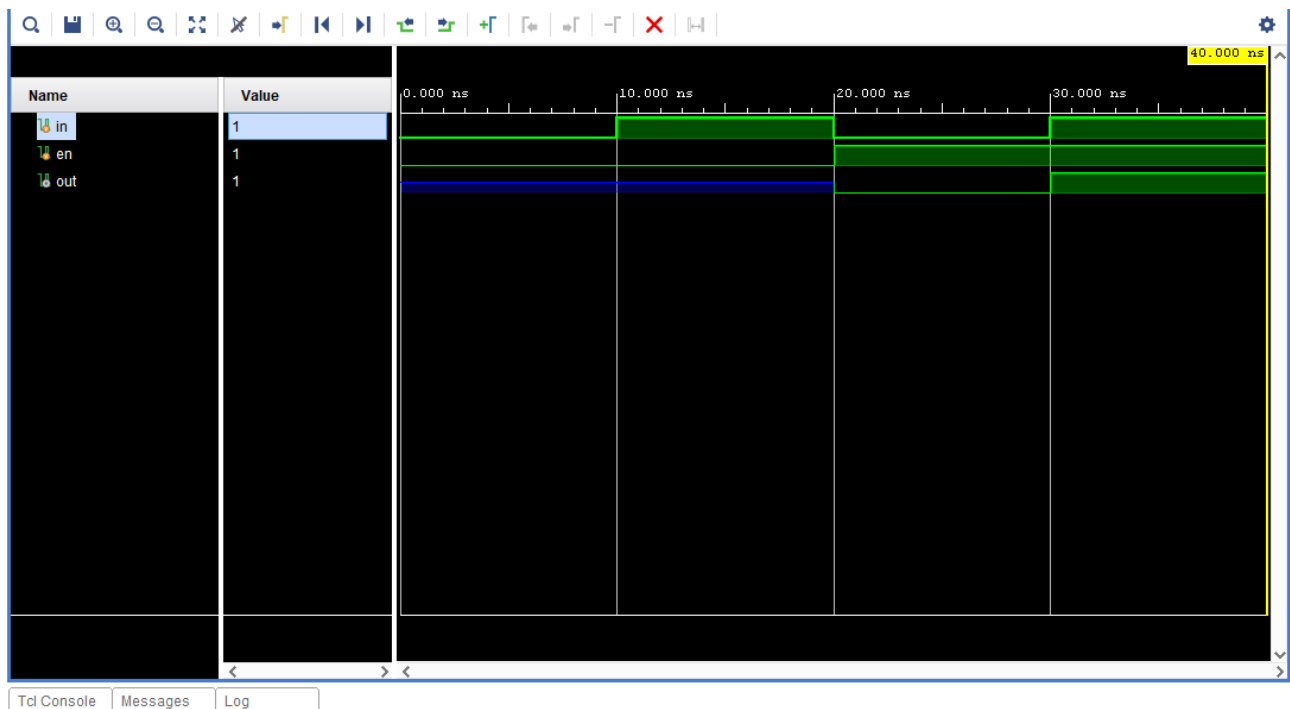
### TestBench:

```
module tb4();  
reg in,en; wire out;  
tristate_buffer uut(in,en,out);  
initial  
begin  
in=0; en=0; #10  
in=1; en=0; #10  
in=0; en=1; #10  
in=1; en=1; #10  
$finish;  
end  
endmodule
```



## 33.RS Latch using NOR gates

### Verilog Code:

```
module srlatch_nor(s,r,qo);  
input s,r;
```

```

output q,qo;
assign q=~(r|qo);
assign qo=~(s|q);
endmodule


```

### **TestBench:**

```

module tb5();
reg s,r;
wire q, qo;
srlatch_nor uut(s,r,q,qo);
initial
begin
s=0; r=0; #10
s=0; r=1; #10
s=1; r=0; #10
s=1; r=1; #10
$finish;
end
endmodule

```

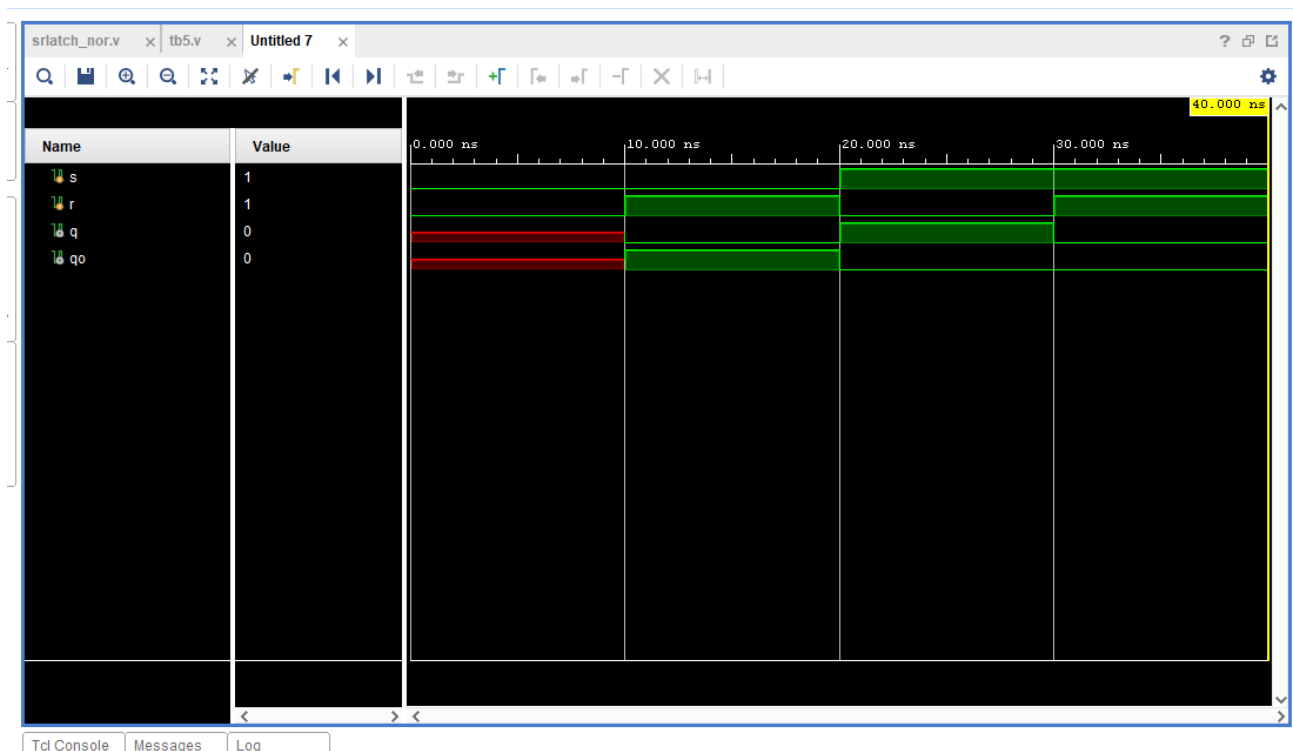

## **34.RS Latch using NAND gates**

### **Verilog Code:**

```

module srlatch_nand(s,r,q,qo);
input s,r;

```

```

inout q,qo;
assign q=~(r&qo);
assign qo=~(s&q);
endmodule


```

## TestBench:

```

module tb6( );
reg s,r;
wire q,qo;
srlatch_nand uut(s,r,q,qo);
initial
begin
s=0; r=0; #10
s=0; r=1; #10
s=1; r=0; #10
s=1; r=1; #10
s=0; r=0; #10
s=1; r=0; #10
s=0; r=1; #10
s=1; r=1; #10
$finish;
end
endmodule

```

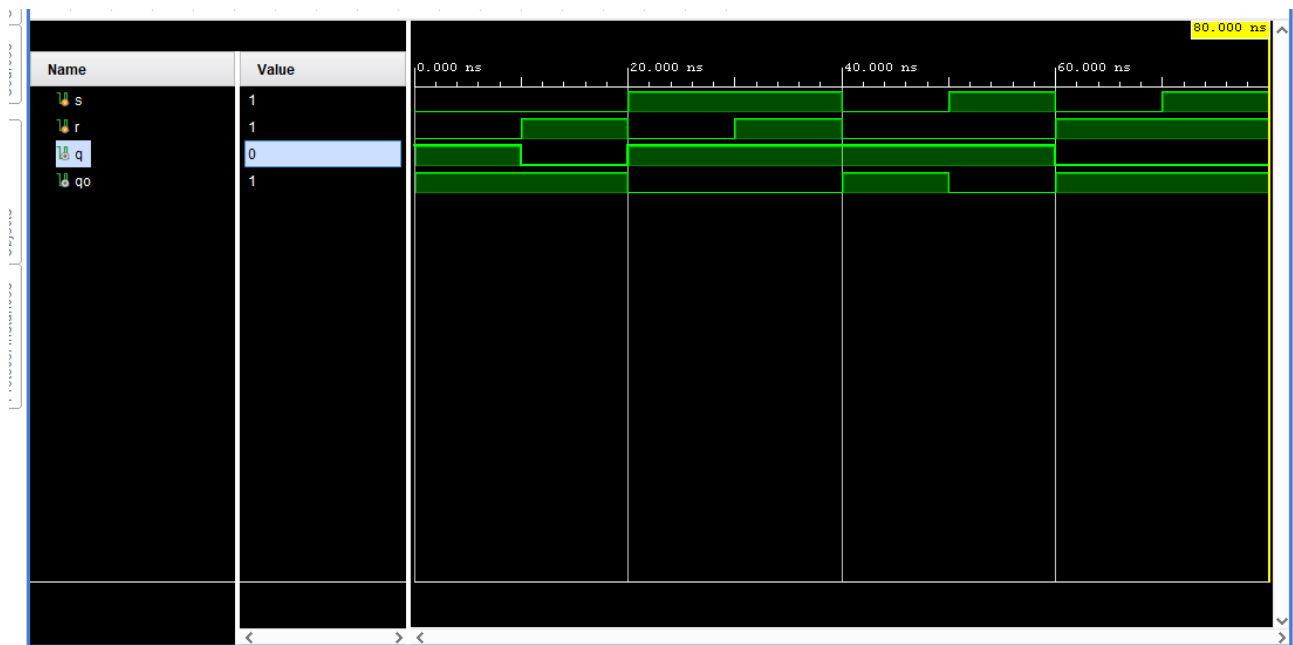

## 35.SR Flipflop

### Verilog Code:

```

module sr_flipflop(clk,s,r,q,qo);
input clk,s,r;
output q,qo;

```



```

assign q=~(s&clk)&qo;
assign qo=~(r&clk)&q;
endmodule


```

### TestBench:

```

module tb7( );
reg clk,s,r; wire q,qo;
sr_flipflop uut(clk,s,r,q,qo);
initial
begin
clk=0;
forever #5 clk=~clk;
end
initial
begin
s=0; r=0; #10
s=0; r=1; #10
s=1; r=0; #10
s=1; r=1; #10
s=0; r=0; #10
s=0; r=1; #10
s=1; r=0; #10
$finish;
end
endmodule

```

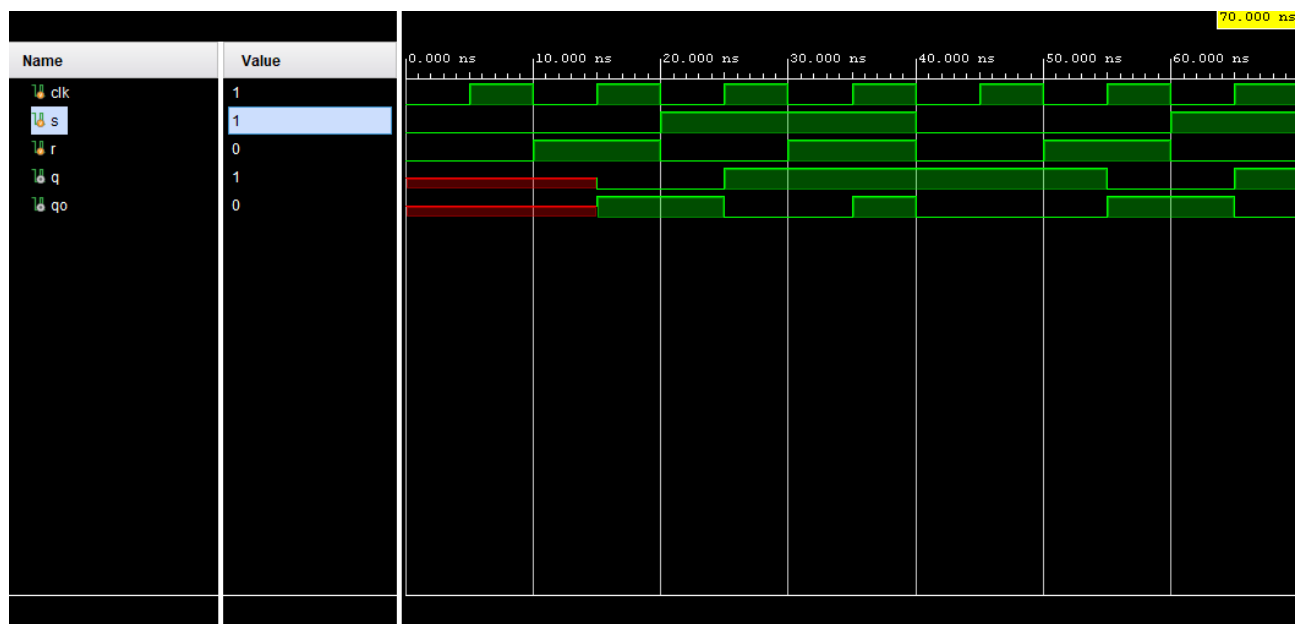

## 36.JK Flipflop

### Verilog Code:

```

module jk_flipflop(j,k,clk,q );
input j,k,clk;

```

```

output reg q;
always @(posedge clk)
begin
case({j,k})
2'b00:q=q;
2'b01:q=1'b0;
2'b10:q=1'b1;
2'b11:q=~q;
endcase
end
endmodule


```

### TestBench:

```

module tb8();
reg clk,j,k;
wire q;
jk_flipflop uut(j,k,clk,q);
initial
begin
clk=0;
forever #5 clk=~clk;
end
initial
begin
j=0; k=0; #10
j=0; k=1; #10
j=1; k=0; #10
j=1; k=1; #10
j=0; k=0; #10
$finish;
end
endmodule

```

 

## 37.D Flipflop

### Verilog Code:

```
module d_flipflop(d,clk,q);
input d,clk;
output reg q;
always @(posedge clk)
begin
case(d)
1'b0: q=0;
1'b1: q=1;
endcase
end
endmodule
```

### TestBench:

```
module tb9();
reg clk,d;
wire q;
d_flipflop uut(d,clk,q);
initial
begin
clk=0;
forever #5 clk=~clk;
end
initial
begin
d=0;#10
d=1;#10
d=0;#10
d=1;#10
d=1;#10
d=0;#10
$finish;
end
endmodule
```



## 38.T Flipflop

### Verilog Code:

```

module t_ff(t,rst,clk,q );
input clk,t,rst;
output reg q;
always@(posedge clk)
begin
if(!rst)
q=1'b0;
else if(t)
q=~q;
end
endmodule

```

### TestBench:

```


module tb10();
reg clk,t,rst;
wire q;
t_ff uut(t,rst,clk,q);
initial
begin
clk=0;
forever #5 clk=~clk;
end
initial
begin

```

```

rst =0;#7
rst=1;t=0; #10
t=1; #10
t=1; #10
rst=0;t=0; #10
rst=1;t=1; #10
t=0; #10
$finish;
end
endmodule

```

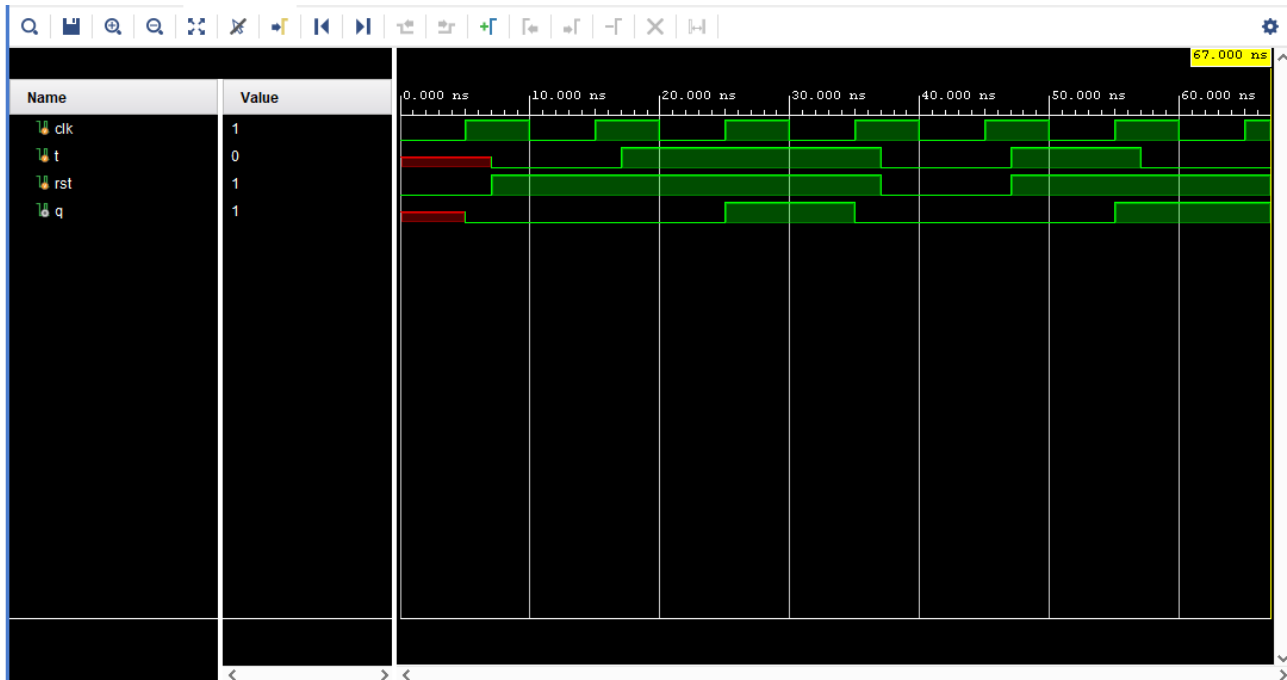

## 39.D Latch

### Verilog Code:

```

module d_latch(d,en,q);
input d,en;
output reg q;
always @(d,en)
begin
if(en)
q=d;
end
endmodule

```

### TestBench:

```


module tb11( );
reg d,en;

```

```

wire q;
d_latch uut(d,en,q);
initial
begin
d=0; en=0; #5
d=1; en=1; #10
d=0; #5
d=1; #5
en=0; d=0; #5
d=1; #5
en=1; d=0; #5
d=1; #5
$finish;
end
endmodule

```

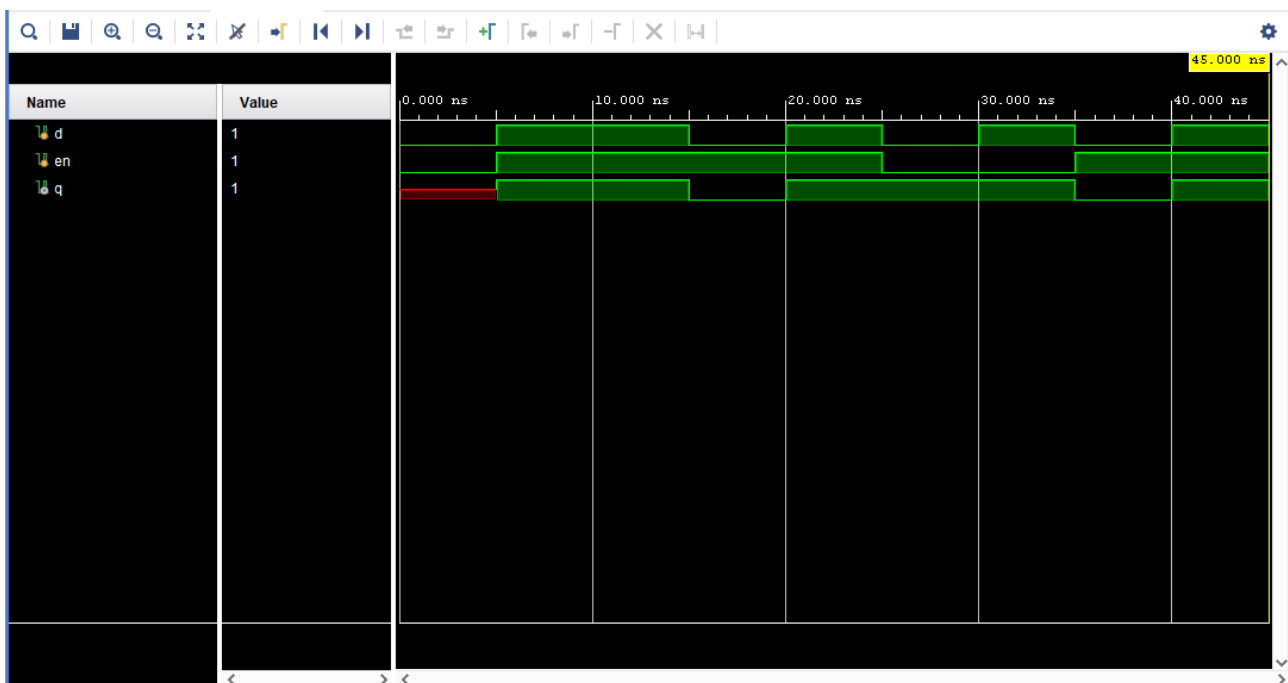

## 40. Asynchronous counter using T Flipflops

### Verilog Code:

```

module t_ff(t,clk,rst,q);
input t,clk,rst;
output reg q;
always @(posedge clk,negedge rst)
begin
if(!rst)
q<=0;
else if(t)
q<=~q;
end


```

```
else  
q<=q;  
end  
endmodule
```

```
module asyn_coun_t_ff(clk,rst,q,qo);  
output [3:0]q;  
output [3:0]qo;  
input clk,rst;  
assign t=1;  
t_ff t1(t,clk,rst,q0);  
t_ff t2(t,q0,rst,q1);  
t_ff t3(t,q1,rst,q2);  
t_ff t4(t,q2,rst,q3);  
assign q={q3,q2,q1,q0};  
assign qo=~q;  
endmodule
```
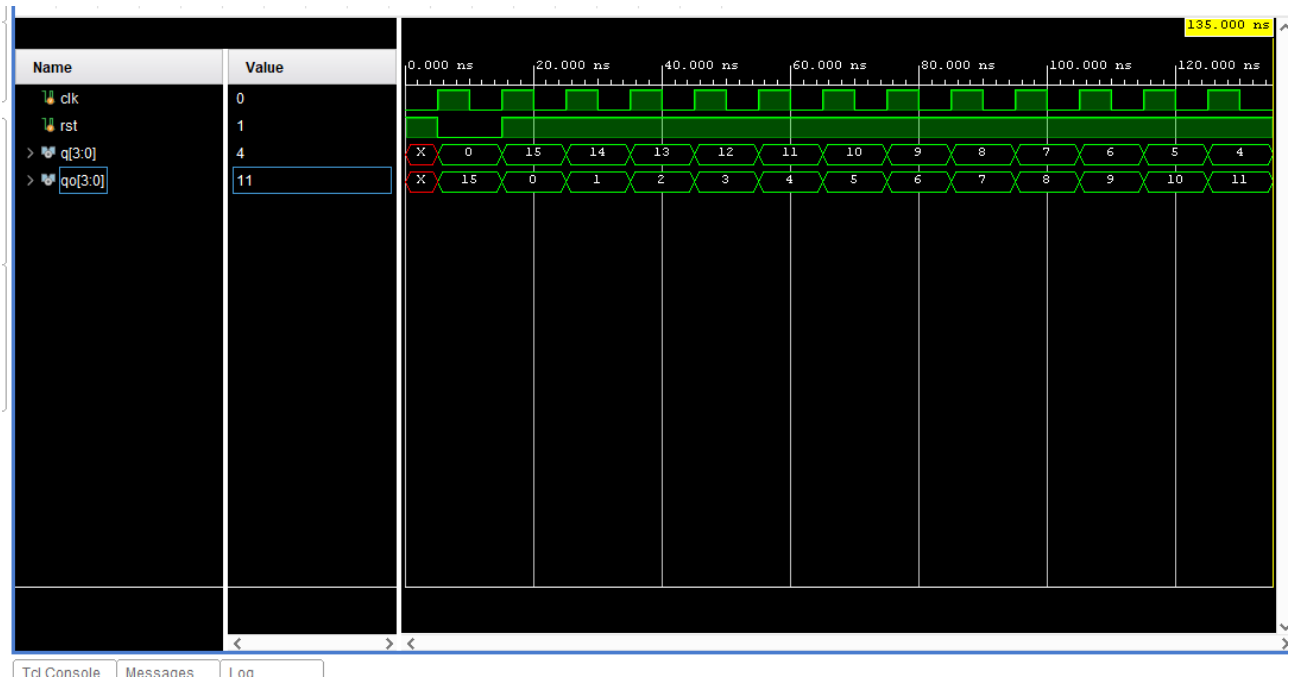
### **TestBench:**

```
module tb2( );  
reg clk,rst;  
wire[3:0]q,qo;  
asyn_coun_t_ff uut(clk,rst,q,qo);  
initial  
begin  
clk=0;  
forever #5 clk=~clk;  
end  
initial  
begin  
rst=1; #5  
rst=0;#10  
rst=1;#120  
$finish;  
end  
endmodule
```



## 41. Synchronous Up and Down Counter

### Verilog Code:

```
module up_down_counter_8(clk,rst,en,out);
input clk,rst,en;
output reg[2:0] out;
always @(posedge clk)
begin
if(!rst)
out=3'b000;
else if (en)
out=out+1;
else
out=out-1;
end
endmodule
```

### TestBench:

```
module tb1();
reg clk,en,rst;
wire[2:0]out;
up_down_counter_8 uut(clk,rst,en,out);
initial
begin
clk=0;
forever #5 clk=~clk;
```




```

end
initial
begin
en=0;rst=1; #5
en=1;rst=0; #5

en=1;rst=1;#85
en=0;rst=1; #90
$finish;
end
endmodule

```

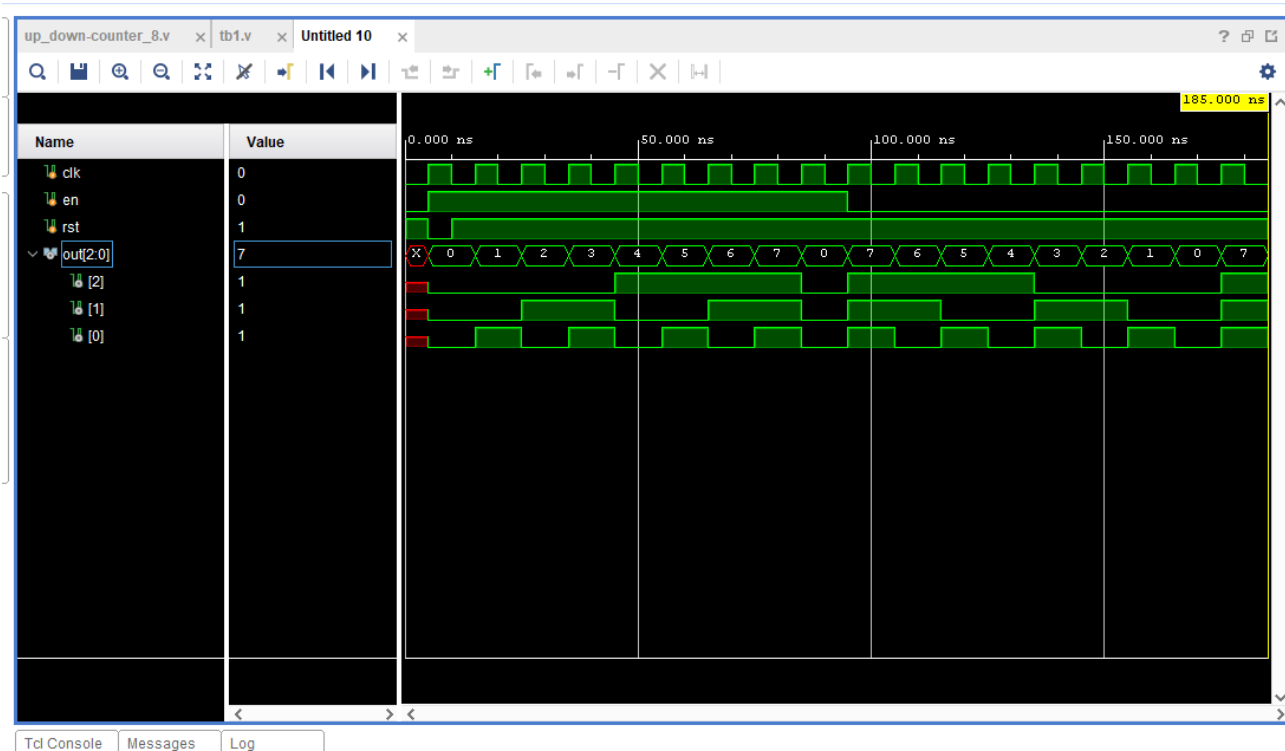

## 42.Johnson Counter

### Verilog Code:


```

module johnson_counter(clk,rst,q);
input clk,rst;
output reg[3:0]q;
always@(posedge clk)
begin
if(!rst)
q<=4'b0000;
else
q<={~q[0],q[3:1]};
end
endmodule

```
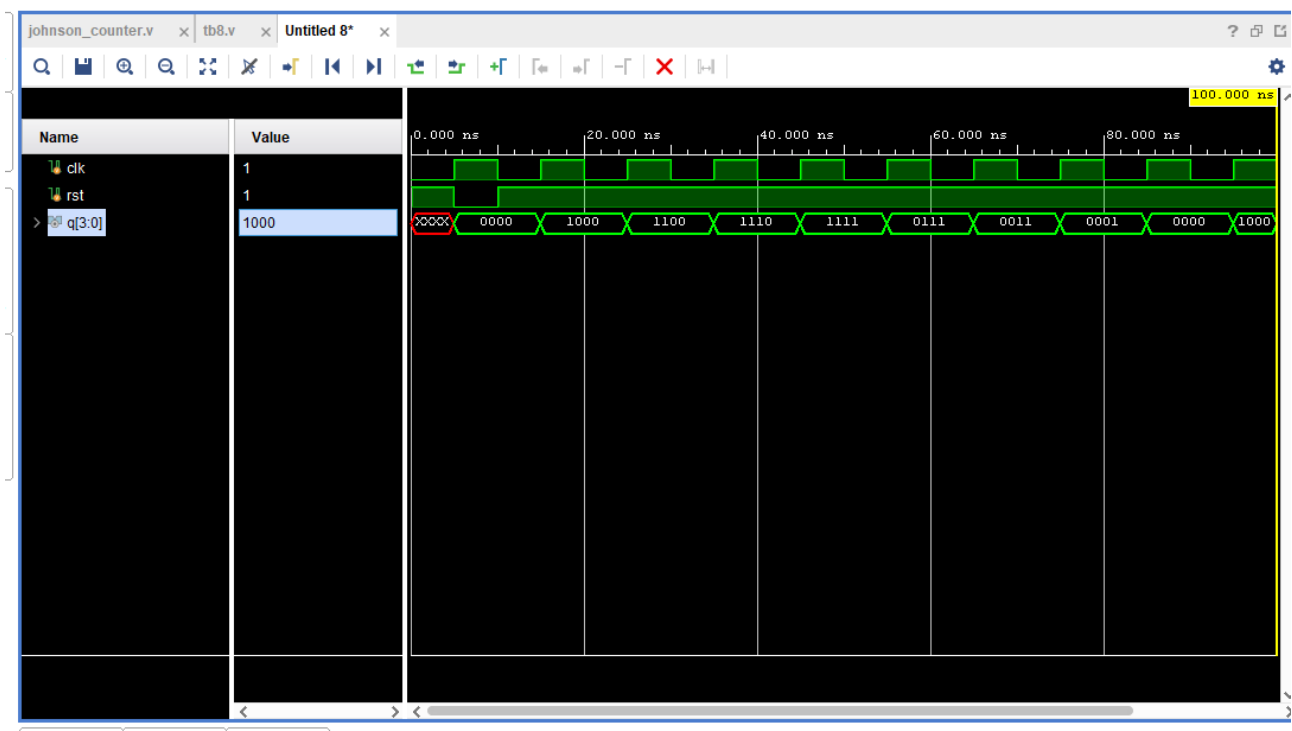
### TestBench:

```
module tb8();  
  reg clk,rst;  
  wire[3:0]q;  
  johnson_counter uut(clk,rst,q);  
  initial  
  begin  
    clk=0;  
    forever #5 clk=~clk;  
  end  
  initial  
  begin  
    rst=1; #5  
    rst=0;#5  
    rst=1; #90  
    $finish;  
  end  
endmodule
```



## 43. Ring Counter

### Verilog Code:

```
module ring_coun_d_ff(clk,rst,q);  
  input clk,rst;  
  output reg[3:0]q;  
  always@(posedge clk)
```

```

begin
if(!rst)
q=4'b0001;
else
q<={q[2:0], q[3]};
end
endmodule


```

### TestBench:

```

module tb3( );
reg clk,rst;
wire [3:0]q;
ring_coun_d_ff uut(clk,rst,q);
initial
begin
clk=0;
forever #5 clk=~clk;
end
initial
begin
rst=1;#5
rst=0;#10
rst=1; #50
$finish;
end
endmodule

```

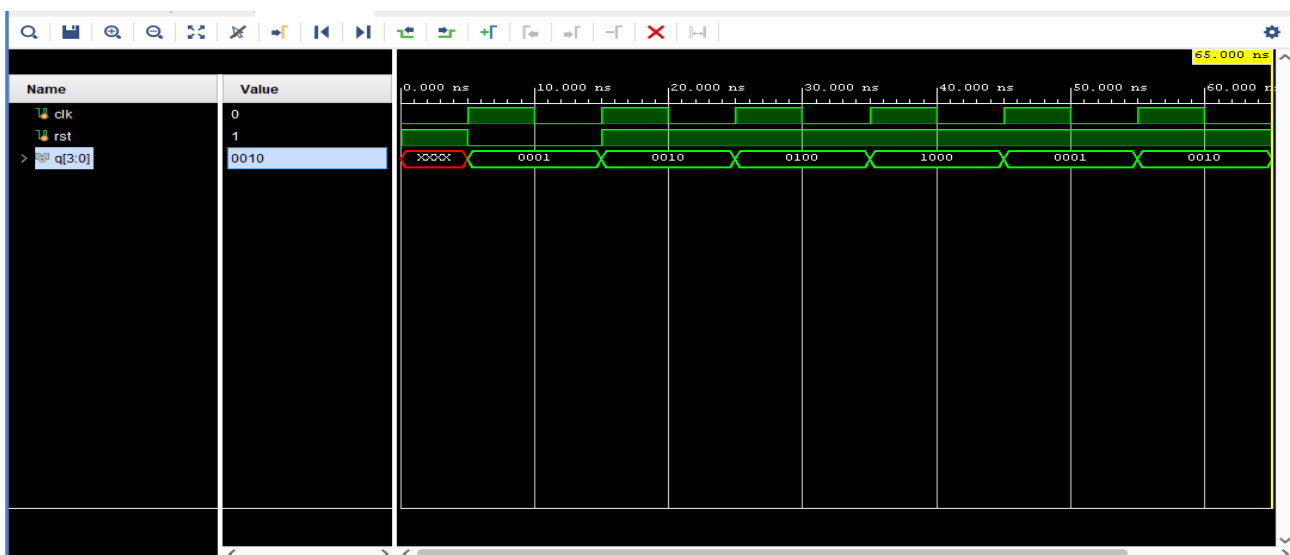

## 44.Serial In Serial Out Shift Register(SISO)

### Verilog Code:

```

module siso(clk,rst,sin,sout );
input clk,sin,rst;

```

```

output sout;
reg[3:0]q;
always @(posedge clk)
begin
if(!rst)
q<=4'b0000;
else
q<={q[2:0],sin};
end
assign sout=q[3];
endmodule


```

### **TestBench:**

```

module tb4();
reg clk,rst,sin;
wire sout;
siso uut(clk,rst,sin,sout);
initial
begin
clk=0;
forever #5 clk=~clk;
end
initial
begin
rst=1; sin=1; #5
rst=0; sin=0; #10
rst=1; sin=1; #10
sin=1; #10
sin=1; #10
sin=0; #10
$finish;
end
endmodule

```

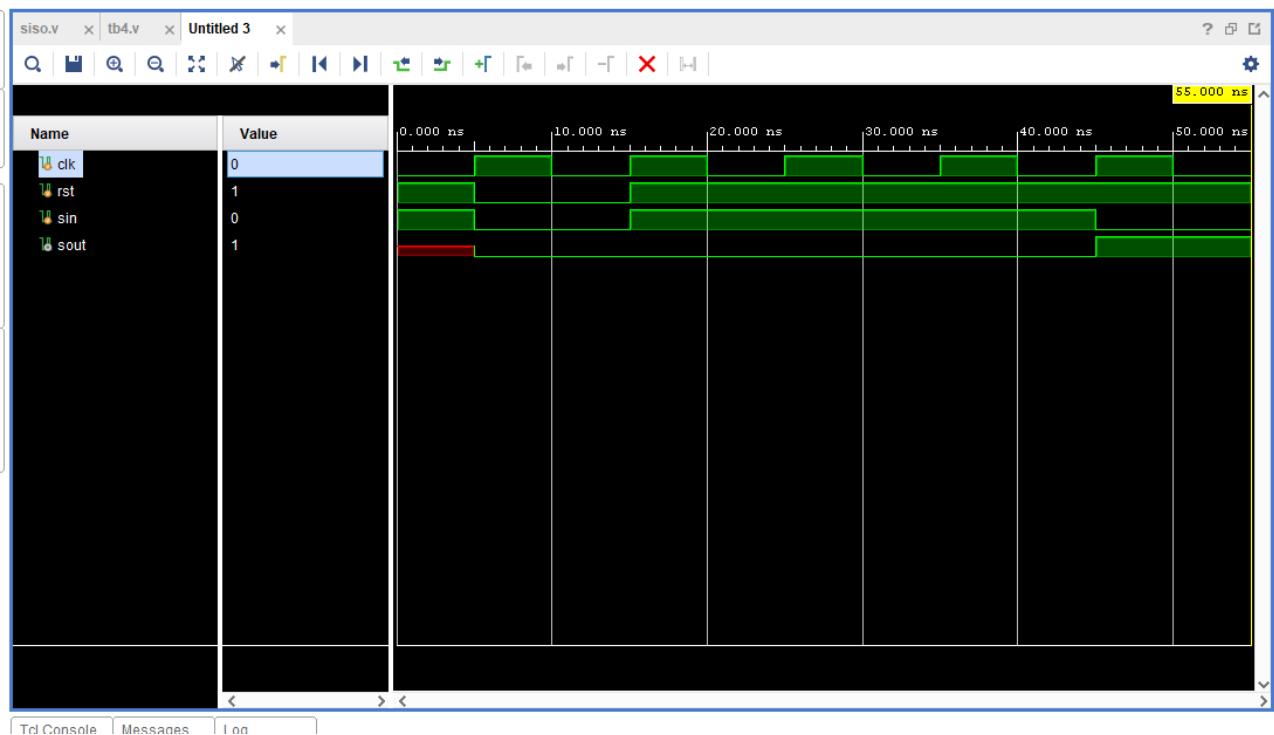

## 45. Serial In Parallel Out Shift Register(SIPO)

### Verilog Code:

```
module sipo(clk,rst,sin,pout );
input clk,sin,rst;
output reg[3:0] pout;
always @(posedge clk)
begin
if(!rst)
pout<=4'b0000;
else
pout<={pout[2:0],sin};
end
endmodule
```


### TestBench:

```
module tb5();
reg clk,rst,sin;
wire[3:0] pout;
sipo uut(clk,rst,sin,pout);
initial
begin
clk=0;
forever #5 clk=~clk;
```

```

end
initial
begin
rst=1; sin=1; #5
rst=0; sin=0; #10
rst=1; sin=1; #10
sin=1; #10
sin=1; #10
sin=0; #10
sin=1; #5
$finish;
end
endmodule

```

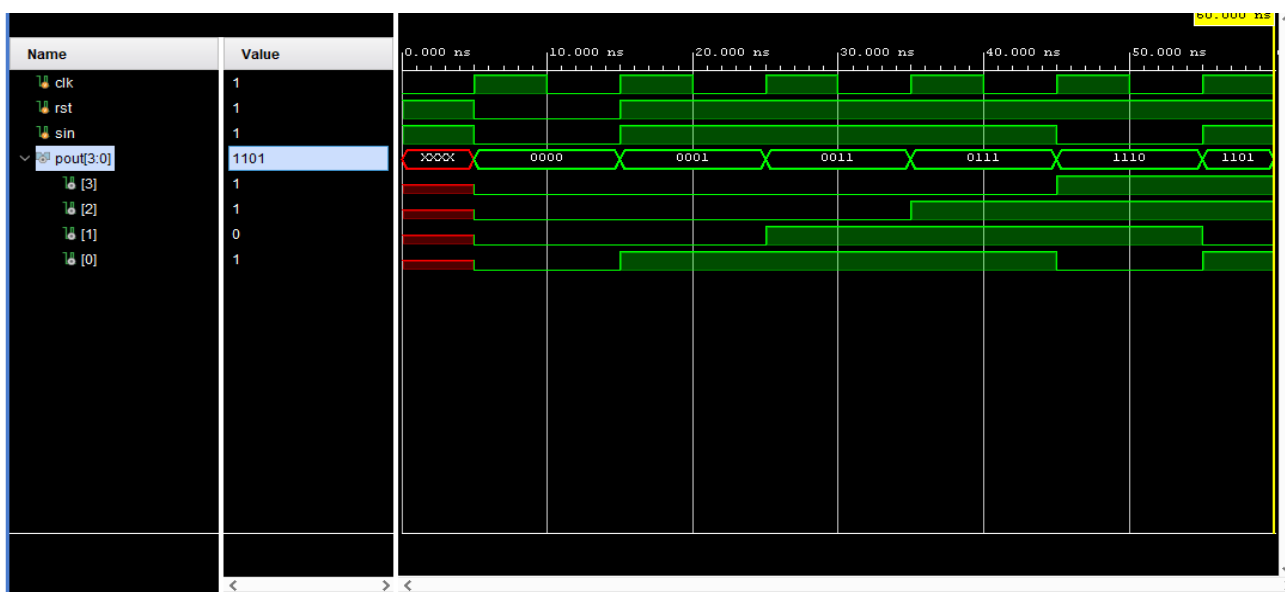

### ***46.Parllel In Serial Out Shift Register(PISO)***

### Verilog Code:

```

module piso(clk,rst,ld,pin,sout );
input clk,rst,ld;
input[3:0] pin;
output sout;
reg[3:0]q;
always @(posedge clk)
begin
if(!rst)
q<=4'b0000;
else if(ld)
q<=pin;
else
q<=(q<<1);

```

```

end
assign sout=q[3];
endmodule


```

### TestBench:

```

module tb6();
reg clk,rst,ld;
reg [3:0]pin;
wire sout;
piso uut(clk,rst,ld,pin,sout);
initial
begin
clk=0;
forever #5 clk=~clk;
end
initial
begin
rst=1;ld=0; pin=4'b1101; #5
rst=0;ld=1; pin=4'b1010; #10
rst=1; pin=4'b0101; #10
pin=4'b1011; #10
pin=4'b1101;ld=0; #10
pin=4'b0000; #10
pin=4'b1101;ld=1; #5
$finish;
end
endmodule

```

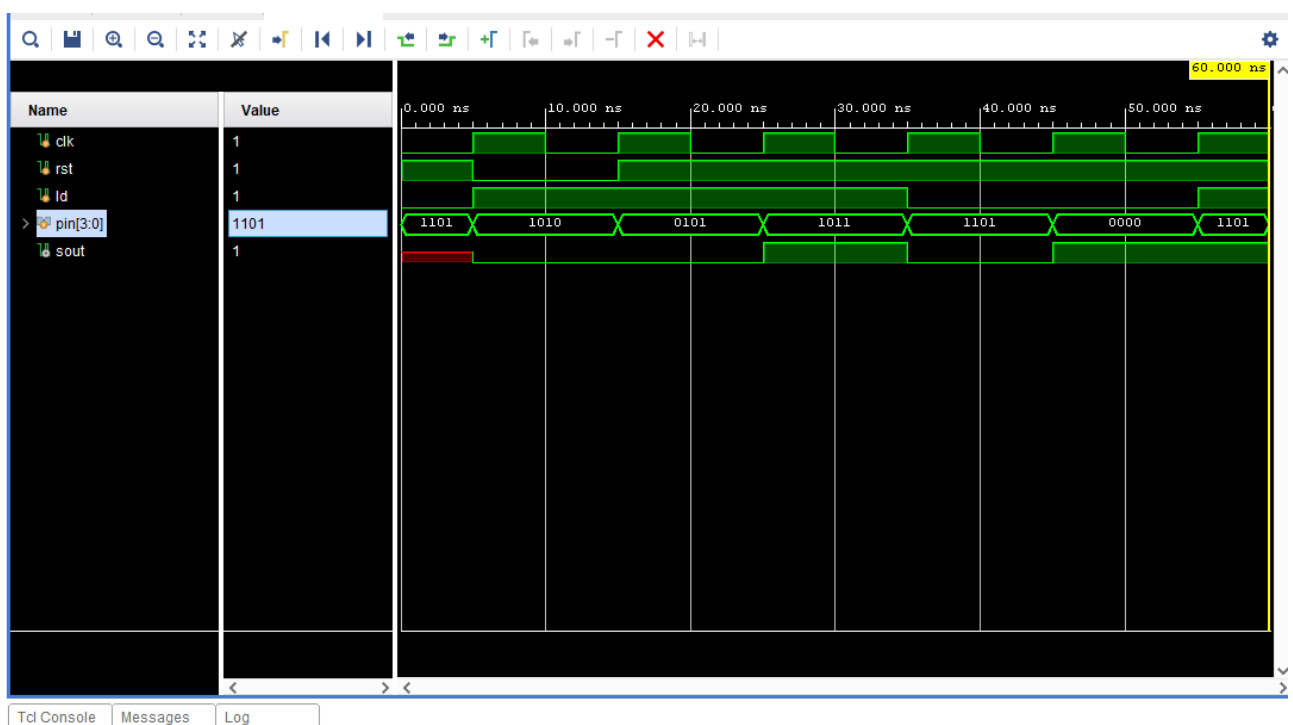

## **47.Parllel In Parllel Out Shift Register(PIPO)**


### **Verilog Code:**

```
module pipo(clk,rst,ld,pin,pout );
input clk,rst,ld;
input[3:0] pin;
output reg[3:0] pout;
always @(posedge clk)
begin
if(!rst)
pout<=4'b0000;
else if(ld)
pout<=pin;
else
pout<=(pout<<1);
end
endmodule
```
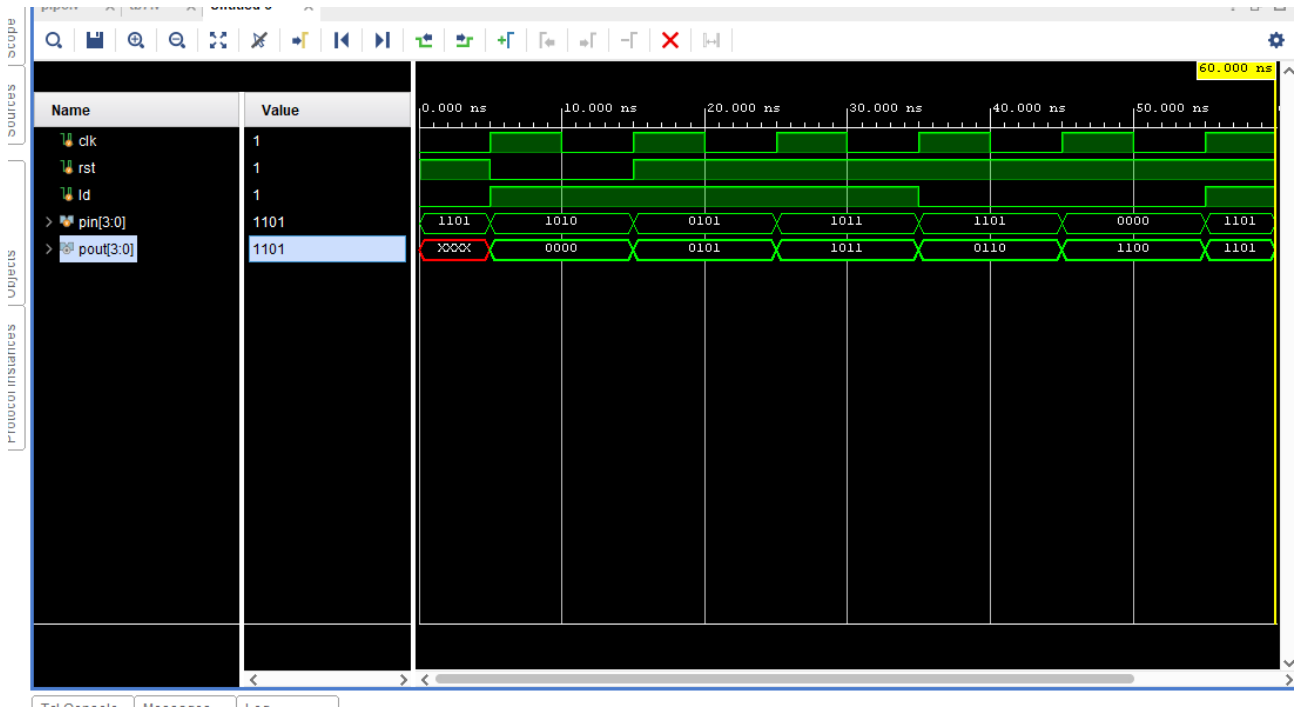
### **TestBench:**

```
module tb7();
reg clk,rst,ld;
reg [3:0]pin;
wire [3:0]pout;
pipo uut(clk,rst,ld,pin,pout);
initial
begin
clk=0;
forever #5 clk=~clk;
end
initial
begin
rst=1;ld=0; pin=4'b1101; #5
rst=0;ld=1; pin=4'b1010; #10
rst=1; pin=4'b0101; #10
pin=4'b1011; #10
pin=4'b1101;ld=0; #10
pin=4'b0000; #10
pin=4'b1101;ld=1; #5
$finish;
end
endmodule
```





## 48.Master-Slave D Flipflop

### Verilog Code:

```

module master_slave_ff(clk,rst,d,master,q);
input clk,d,rst;
output reg q;
output reg master;
always@(posedge clk,negedge rst)
begin
if(!rst)
master<=0;
else
master<=d;
end
always@(negedge clk,negedge rst)
begin
if(!rst)
q<=0;
else
q<=master;
end
endmodule

```

### TestBench:

```


module tb9();
reg clk,rst,d;
wire master,q;

```

```

master_slave_ff uut(clk,rst,d,master,q);
initial
begin
clk=0;
forever#5 clk=~clk;
end
initial
begin
d=1;rst=1; #10
d=1;rst=0; #5
d=1;rst=1; #10
d=0;rst=1; #10
d=1;rst=1; #10
d=0;rst=1; #10
d=1;rst=1; #10
$finish;
end
endmodule

```

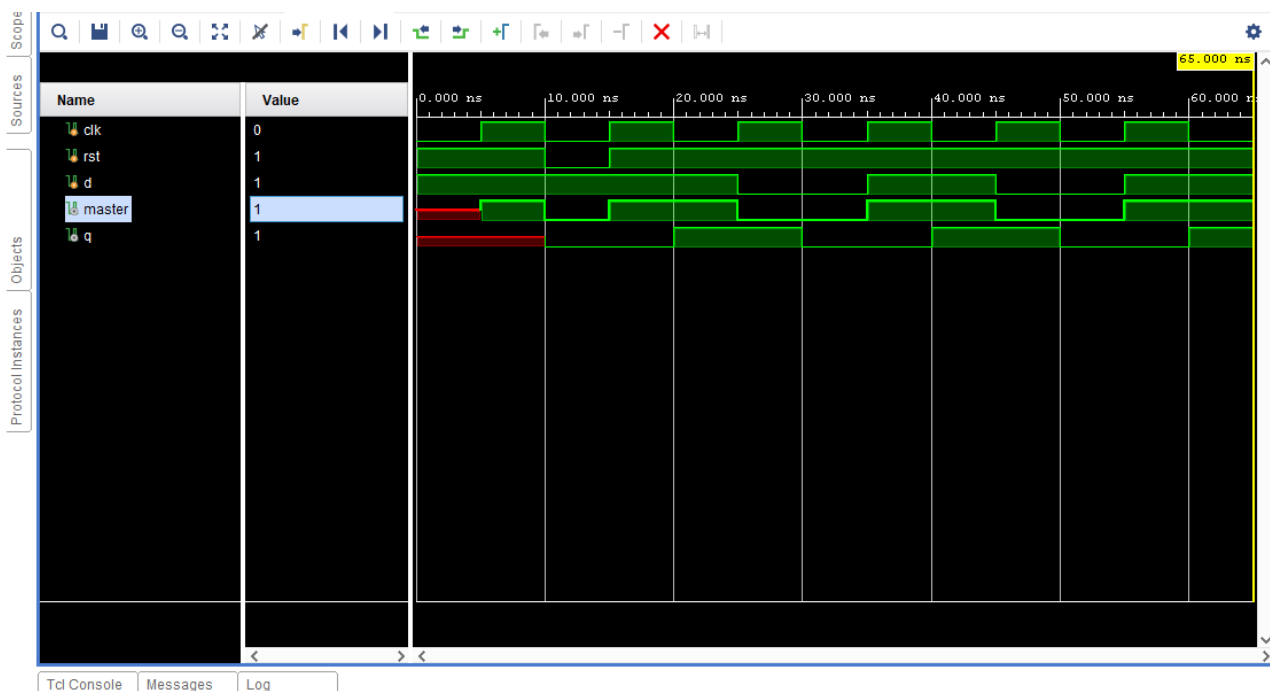

## 49.Sequence Detector using Mealy FSM

### Verilog Code:

```

module seq_det_mealy ( clk,rst, in,out);
input clk,rst, in;
output reg out;
reg [1:0] state, next_st;
parameter s0 = 2'b00, s1 = 2'b01,s2 = 2'b10,s3 = 2'b11;
always @(posedge clk or negedge rst)

```

```

begin
if (!rst)
state <= s0;
else
state <= next_st;
end
always @(*) begin
case (state)
s0: begin
next_st = in ? s1 : s0;
out = 0;
end
s1: begin
next_st = in ? s1 : s2;
out = 0;
end
s2: begin
next_st = in ? s3 : s0;
out = 0;
end
s3: begin
next_st = in ? s1 : s2;
out = in ? 1 : 0;
end
default: begin
next_st = s0;
out = 0;
end
endcase
end
endmodule

```

### **TestBench:**

```


module tb10();
reg clk,rst, in;
wire out;
seq_det_mealy uut(clk,rst,in,out);
initial
begin
clk=0;
forever#5 clk=~clk;
end
initial
begin
in=1; rst=1; #5

```

```

in=0;rst=0;#5
in=1; rst=1; #5
in=0; #10
in=1; #10
in=0; #10
in=1; #10
in=1; #10
in=0; #10
in=1; #10
in=1; #10
in=0; #10
$finish;
end
endmodule

```

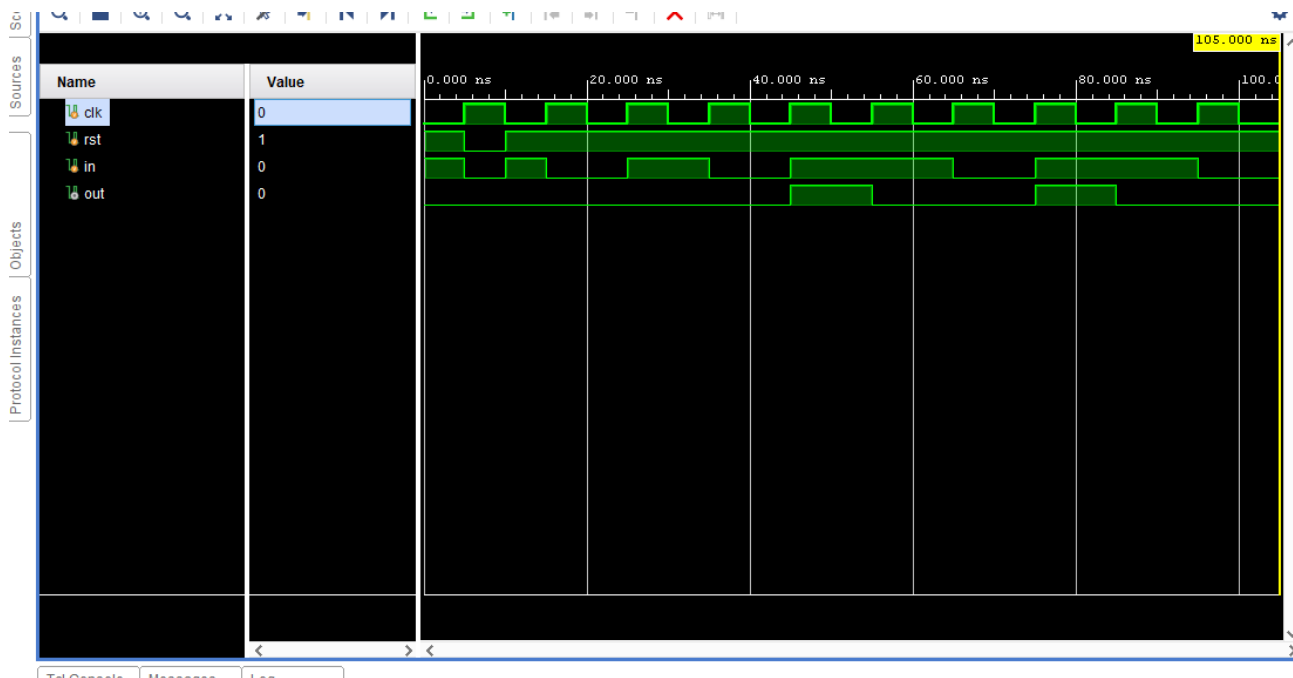

## 50.Sequence Detector using Moore FSM

### Verilog Code:

```

module seq_det_moore(clk,rst,in,out);
input clk,rst,in;
output reg out;
reg [2:0] state, next_st;
parameter s0 = 3'b000, s1 = 3'b001,s2 = 3'b010,s3 = 3'b011,s4=3'b100;
always @(posedge clk or negedge rst)
begin
if (!rst)
state <= s0;
else

```

```

state <= next_st;
end
always @(*) begin
case (state)
s0: begin
next_st = in ? s1 : s0;
out = 0;
end
s1: begin
next_st = in ? s1 : s2;
out = 0;
end
s2: begin
next_st = in ? s3 : s0;
out = 0;
end
s3: begin
next_st = in ? s4 : s2;
out = 0;
end
s4: begin
next_st = in ? s1 : s2;
out = 1;
end
default: begin
next_st = s0;
out = 0;
end
endcase
end
endmodule

```

### **TestBench:**

```


module tb11();
reg clk,rst, in;
wire out;
seq_det_moore uut(clk,rst,in,out);
initial
begin
clk=0;
forever#5 clk=~clk;
end
initial
begin
in=1; rst=1; #5

```

```

in=0;rst=0;#5
in=1; rst=1; #15
in=0; #10
in=1; #10
in=1; #10
in=0; #10
in=1; #10
in=1; #20
in=0; #10
in=1; #10
in=1; #10
$finish;
end
endmodule

```

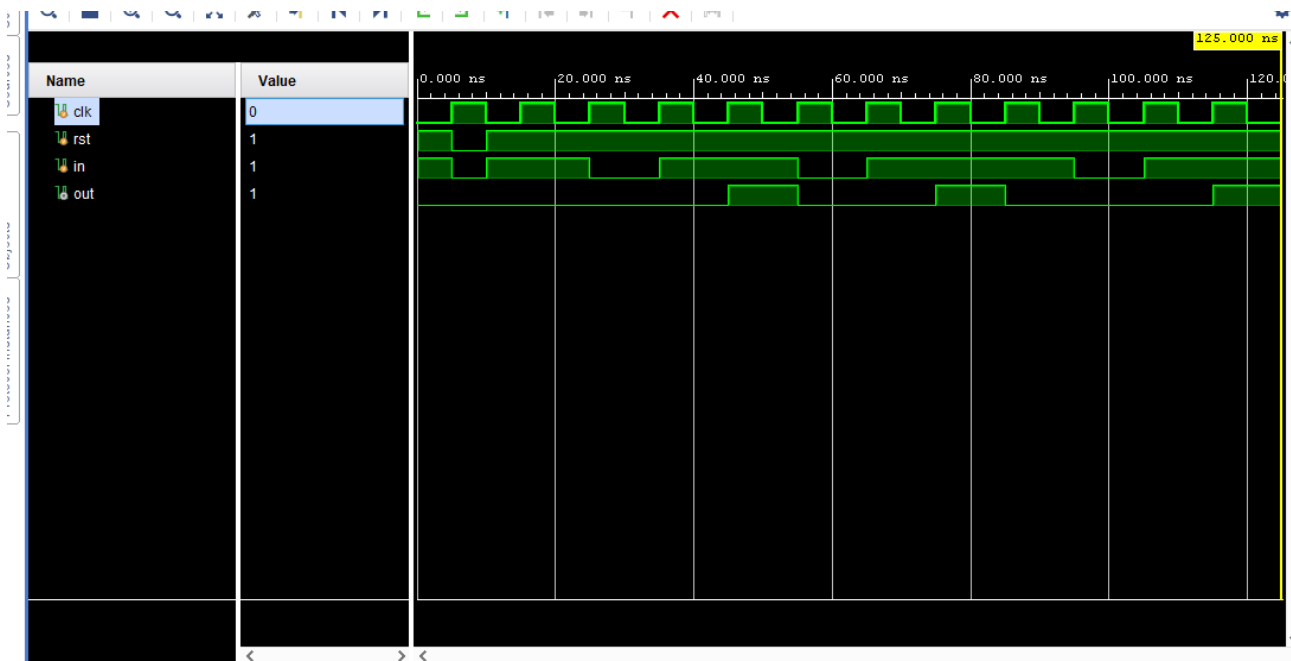

# Thankyou

\_SuryaPrakashTamma  
 n200122@rguktn.ac.in